Imperial College London

Lecture 5


Combinational Circuits

Prof Peter YK Cheung


Department of Electrical & Electronic Engineering

URL: https://elec50010-iac.github.io/course-website/
email: p.cheung@imperial.ac.uk

XOR gate explained (1)

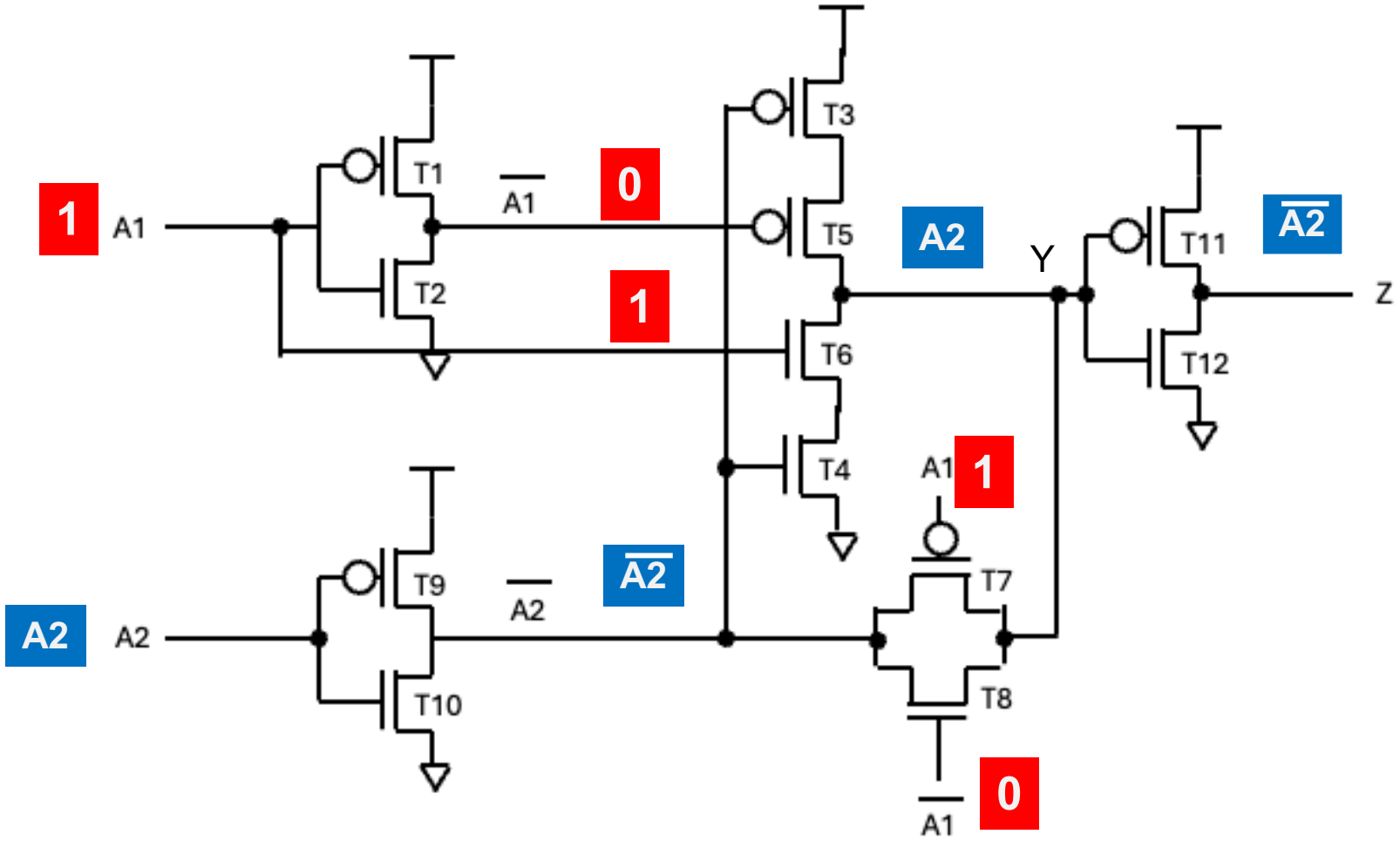


XOR gate explained (2)

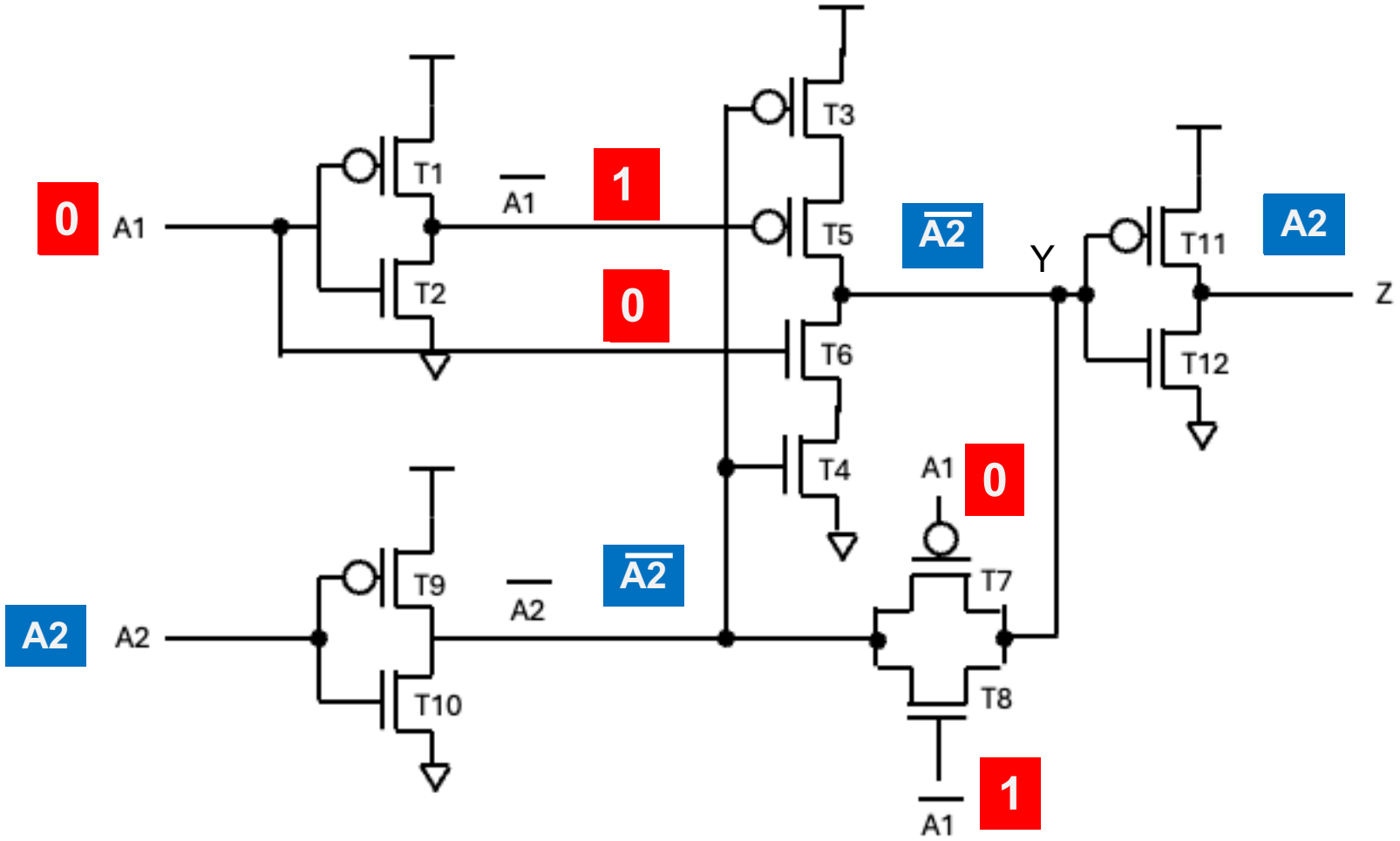


Compound Gates

Unit Inverter

$Y = \overline{A}$

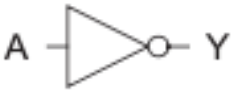


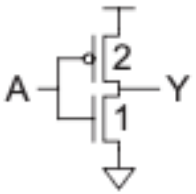

AOI21


$Y = \overline{A \cdot B + C}$




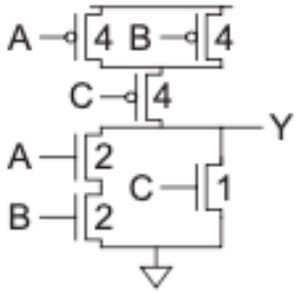

AOI22

$Y = \overline{A \cdot B + C \cdot D}$

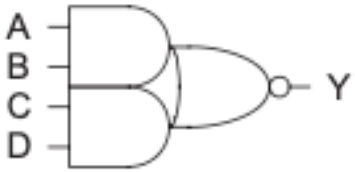

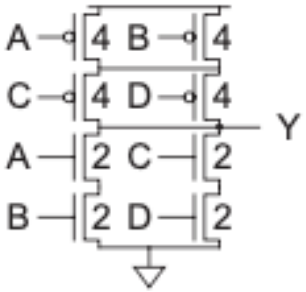


W&H p330


vsclib Standard Cell Library – aoi21






```
z:
((a1*a2)+b)'
```

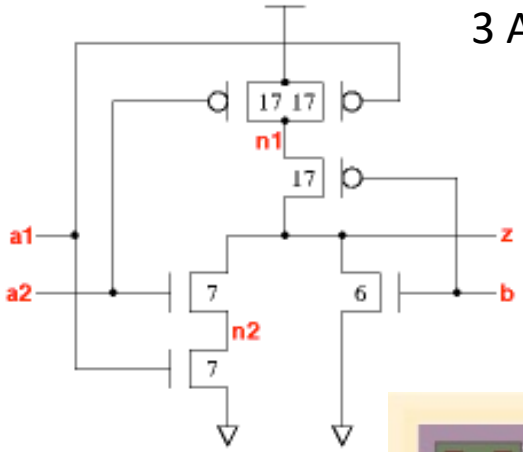
3 AOI31 cells with different drive strengths.




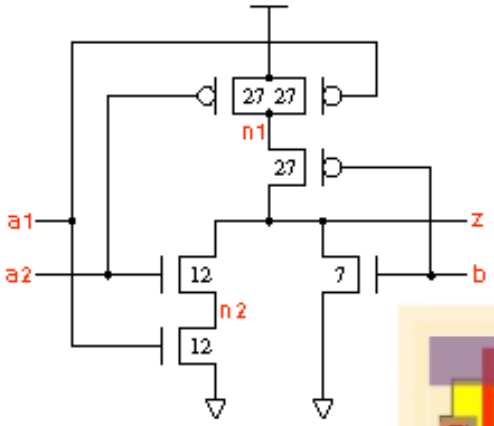

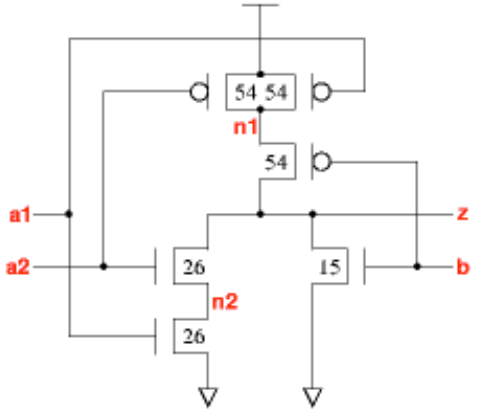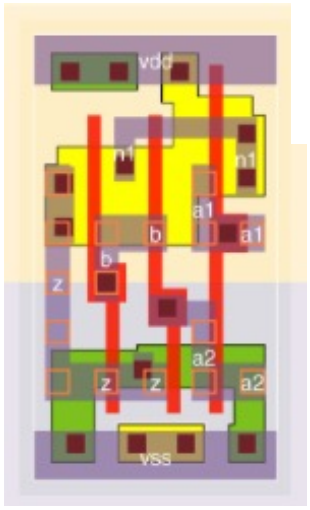





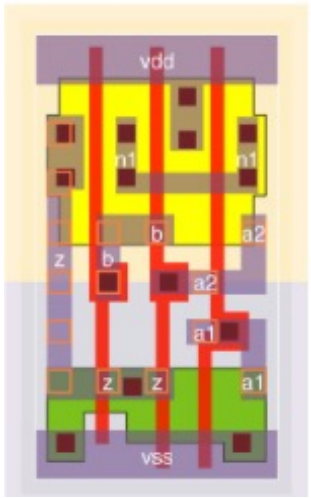

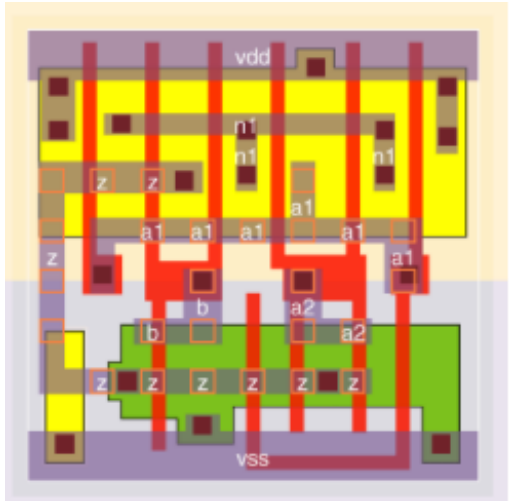


Complex Compound Gate

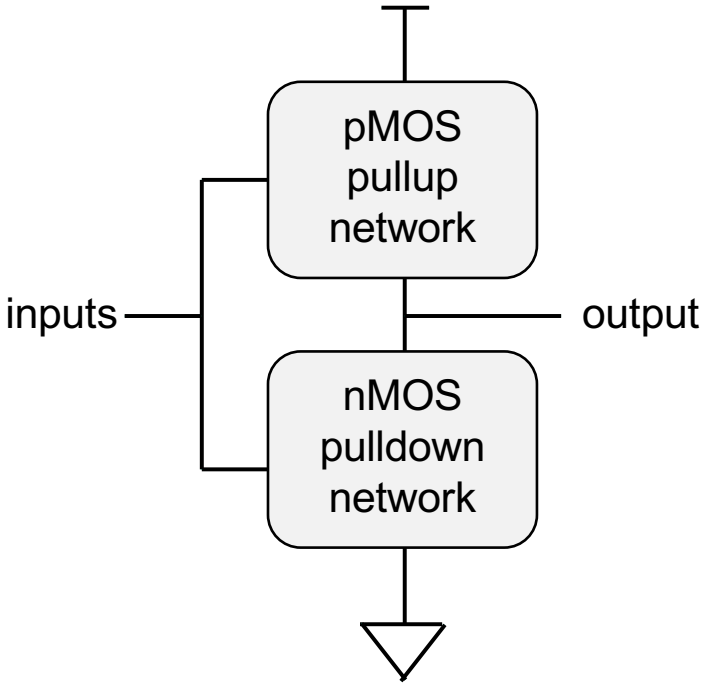

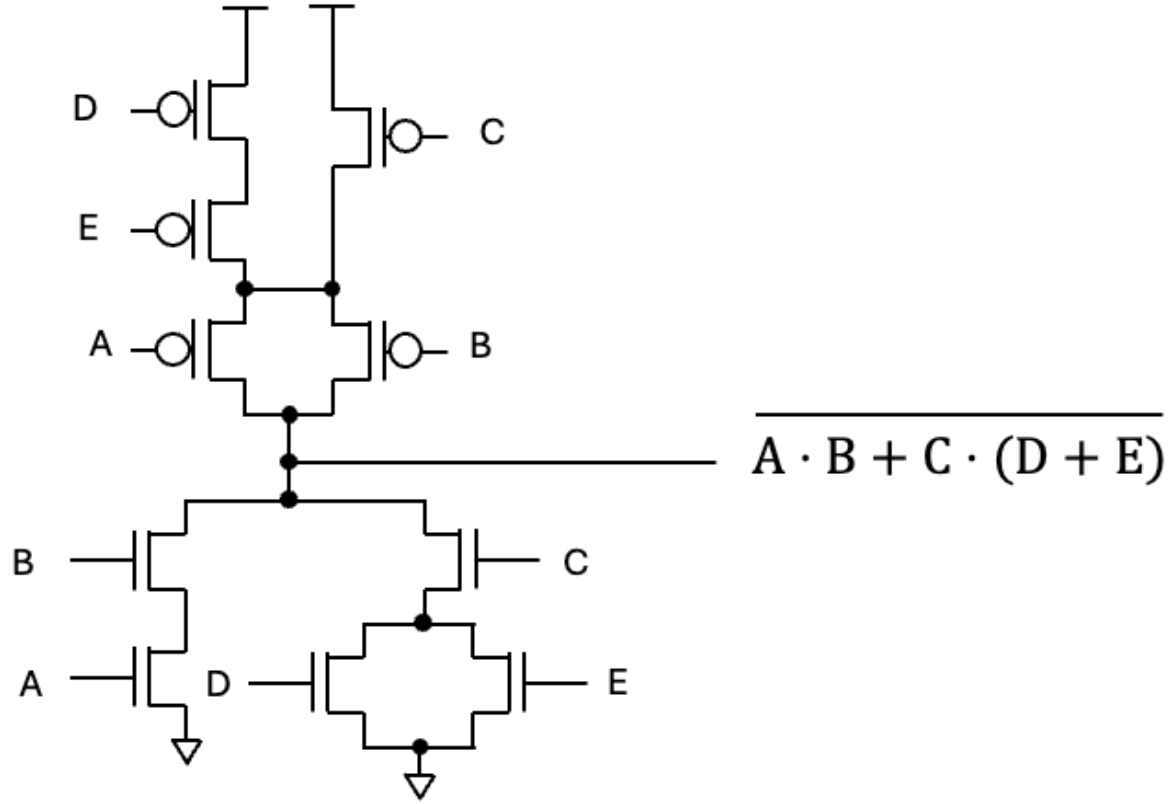


$$\overline{A \cdot B + C \cdot (D + E)}$$

Pseudo-nMOS Logic Gates

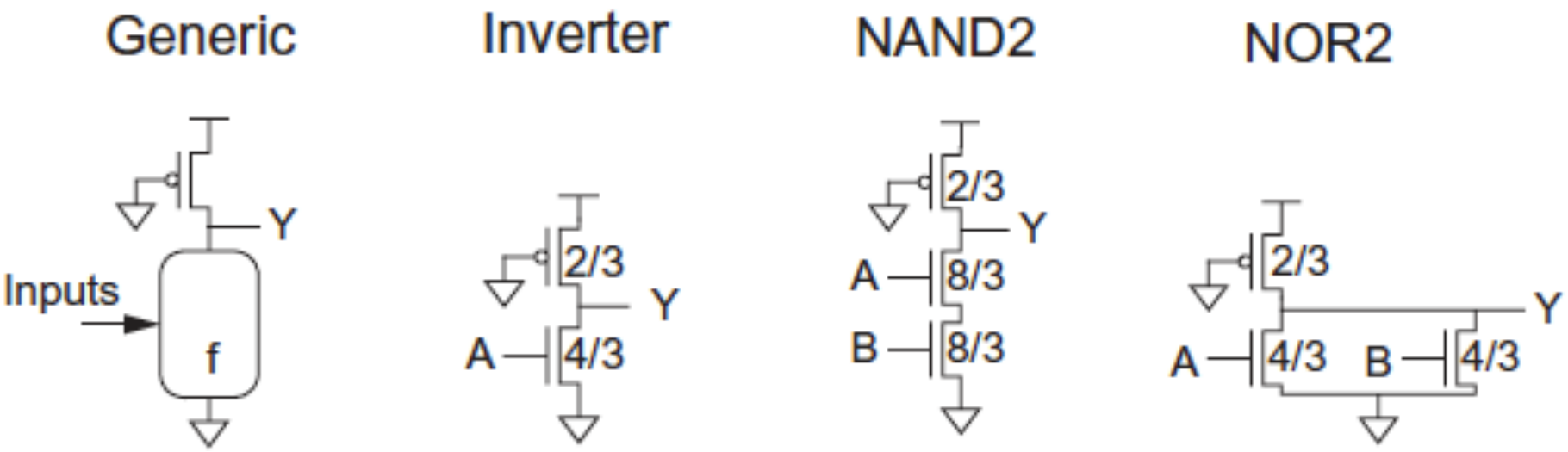


W&H p335-336


Dynamic Logic Gates

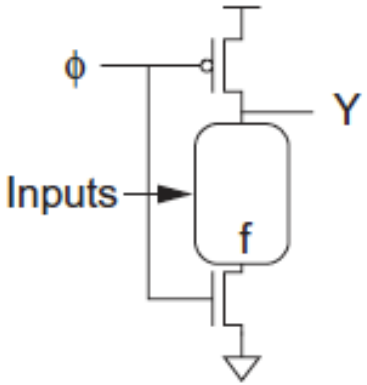



Footed

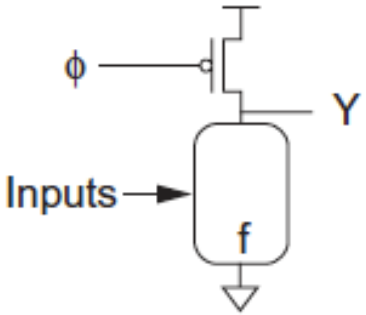


Unfooted

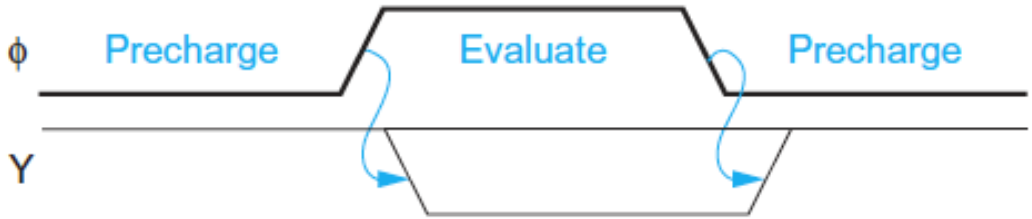

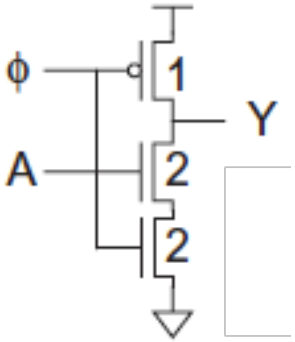


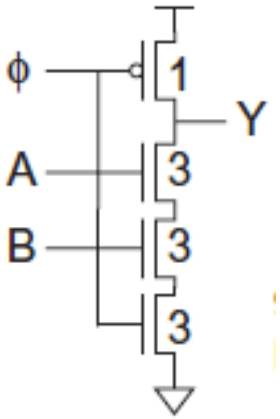


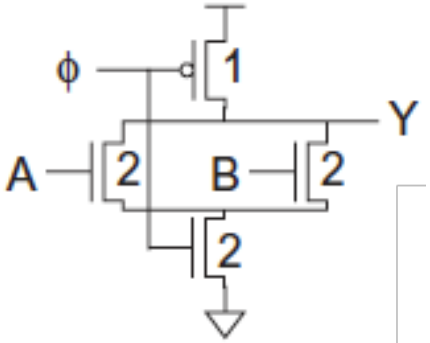

W&H p339-341


Problem with Dynamic Logic Gates

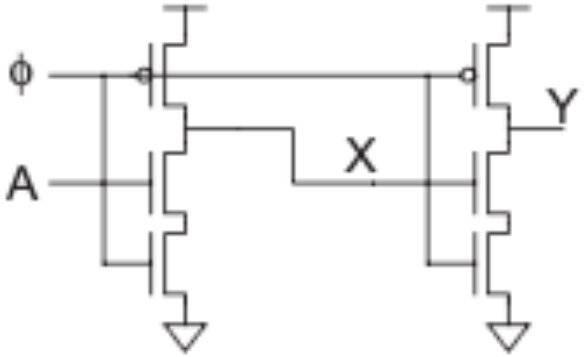


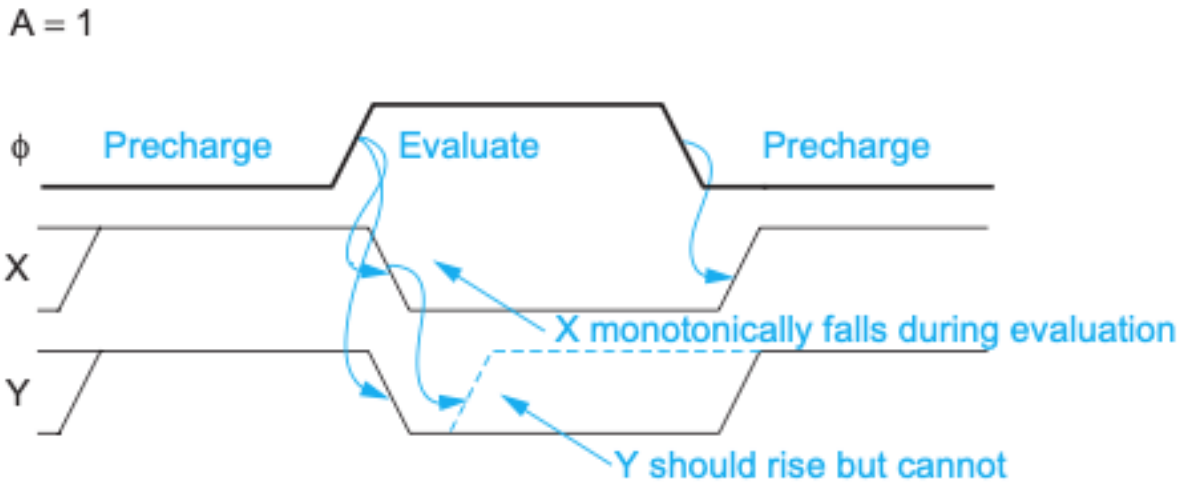


W&H p341

Domino Logic

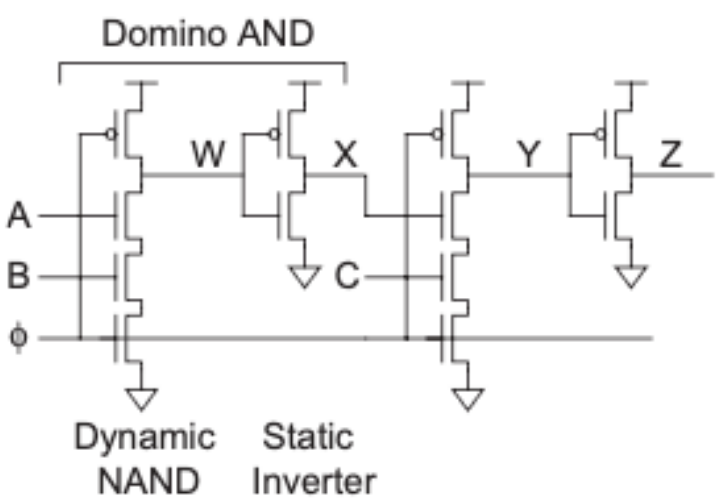


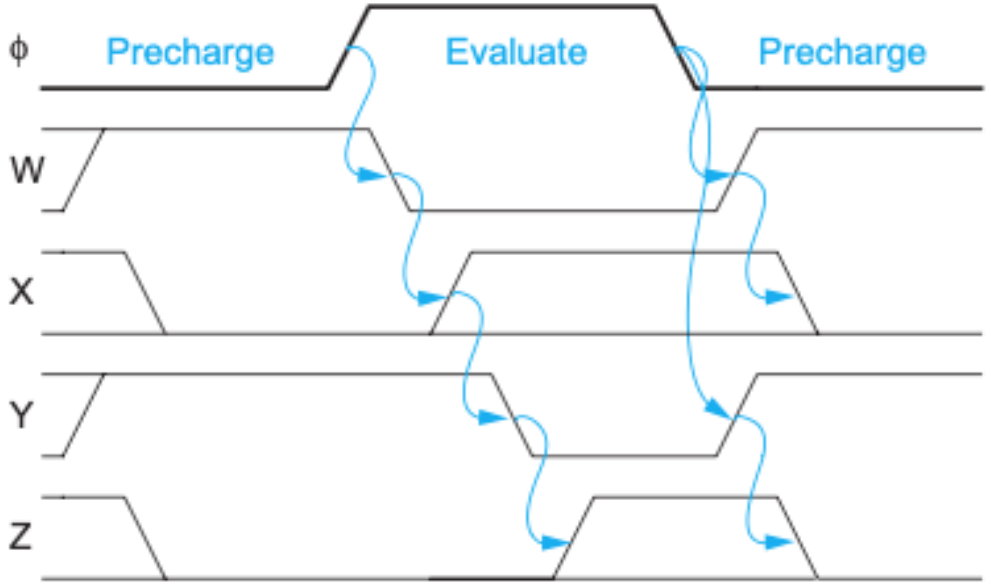


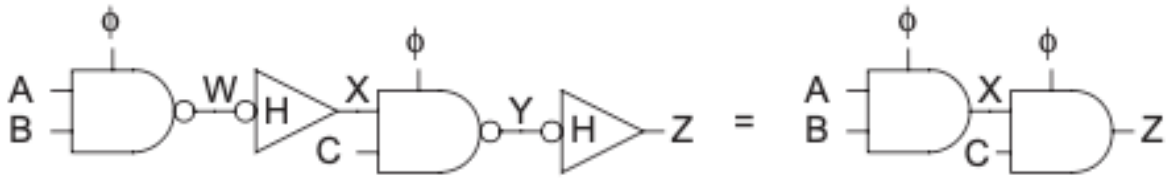



W&H p341-342

Keepers for Dynamic Logic

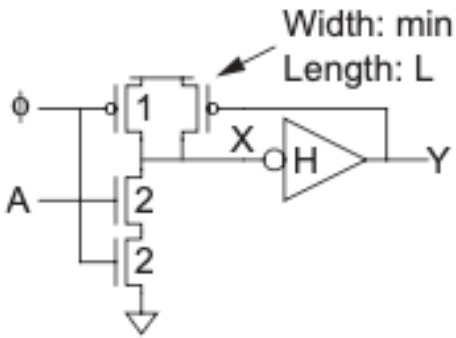

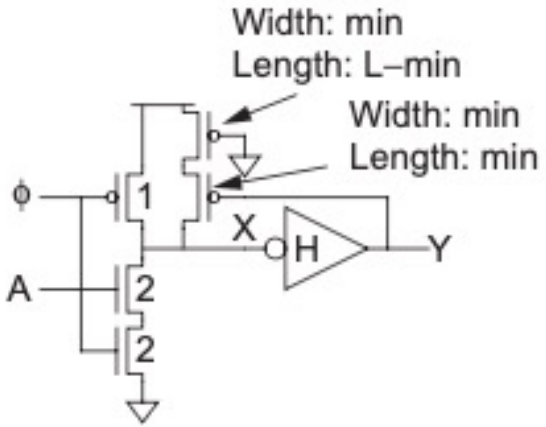


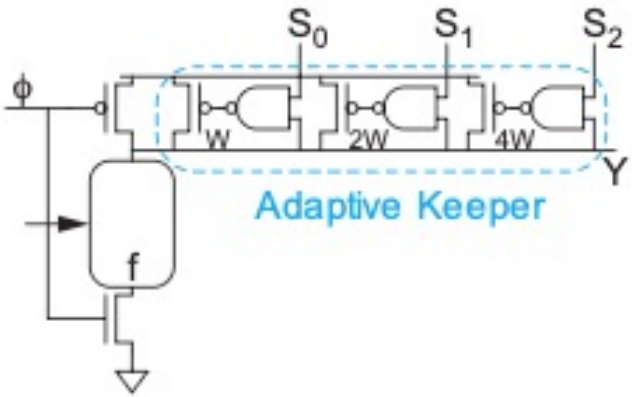


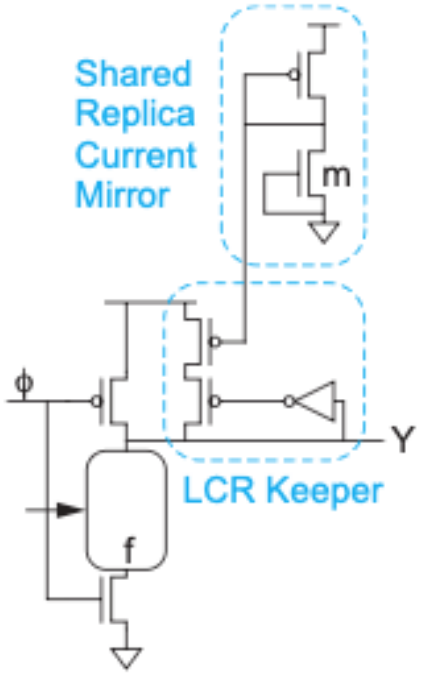


W&H p343-344

Charge Sharing in Dynamic logic

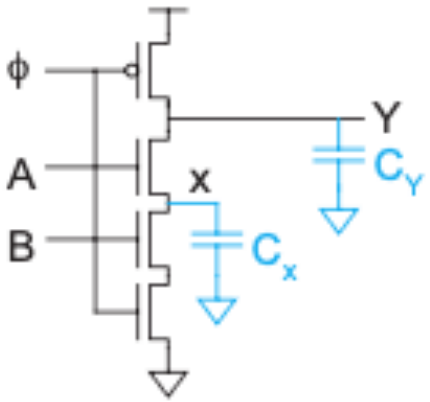

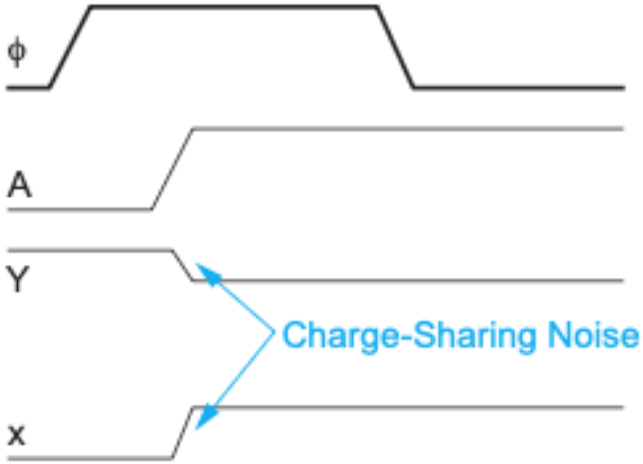

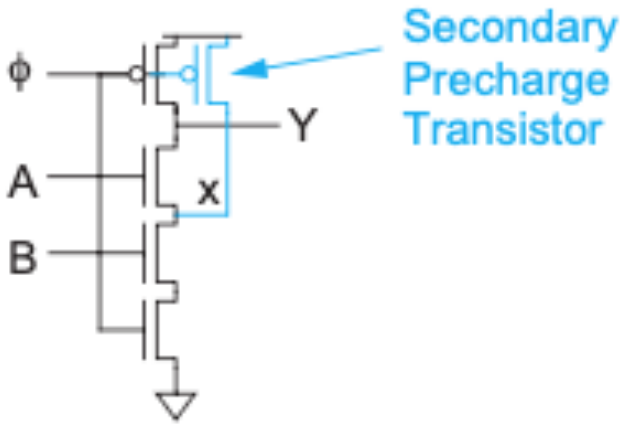

W&H p345