Imperial College London

Lecture 7


Array Subsystems

Prof Peter YK Cheung

Department of Electrical & Electronic Engineering


URL: https://elec70142-digital-vlsi-design.github.io/course-website/
E-mail: p.cheung@imperial.ac.uk


Categories of Memory Arrays

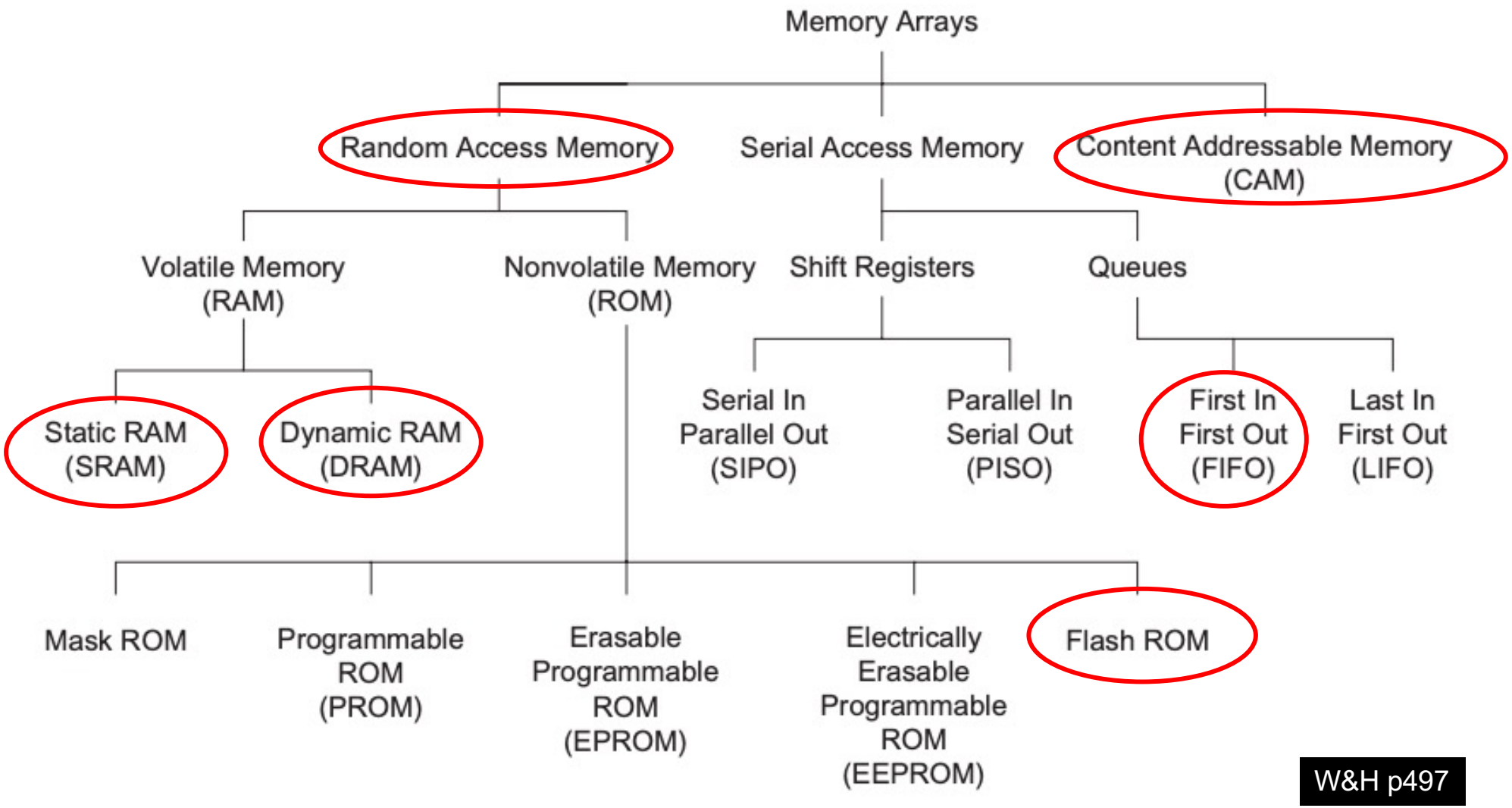

W&H p497


Memory Array Architecture

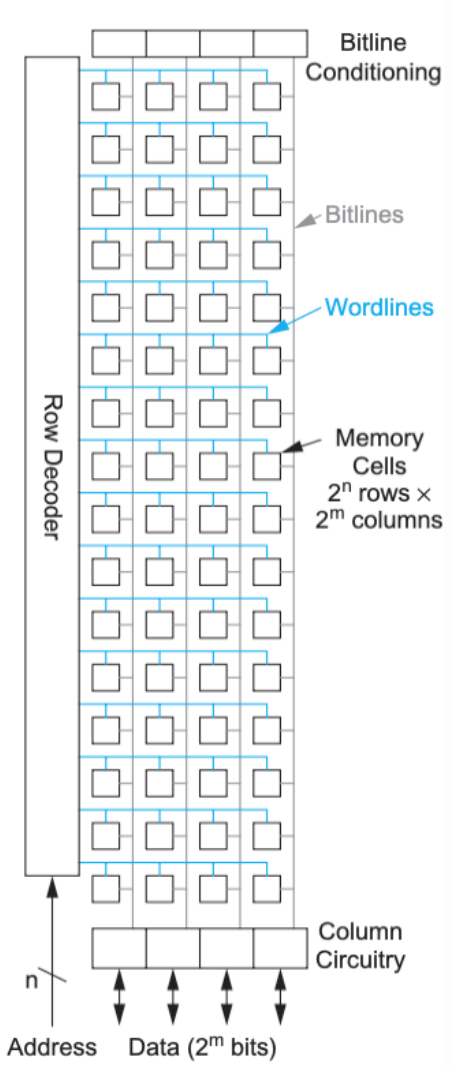


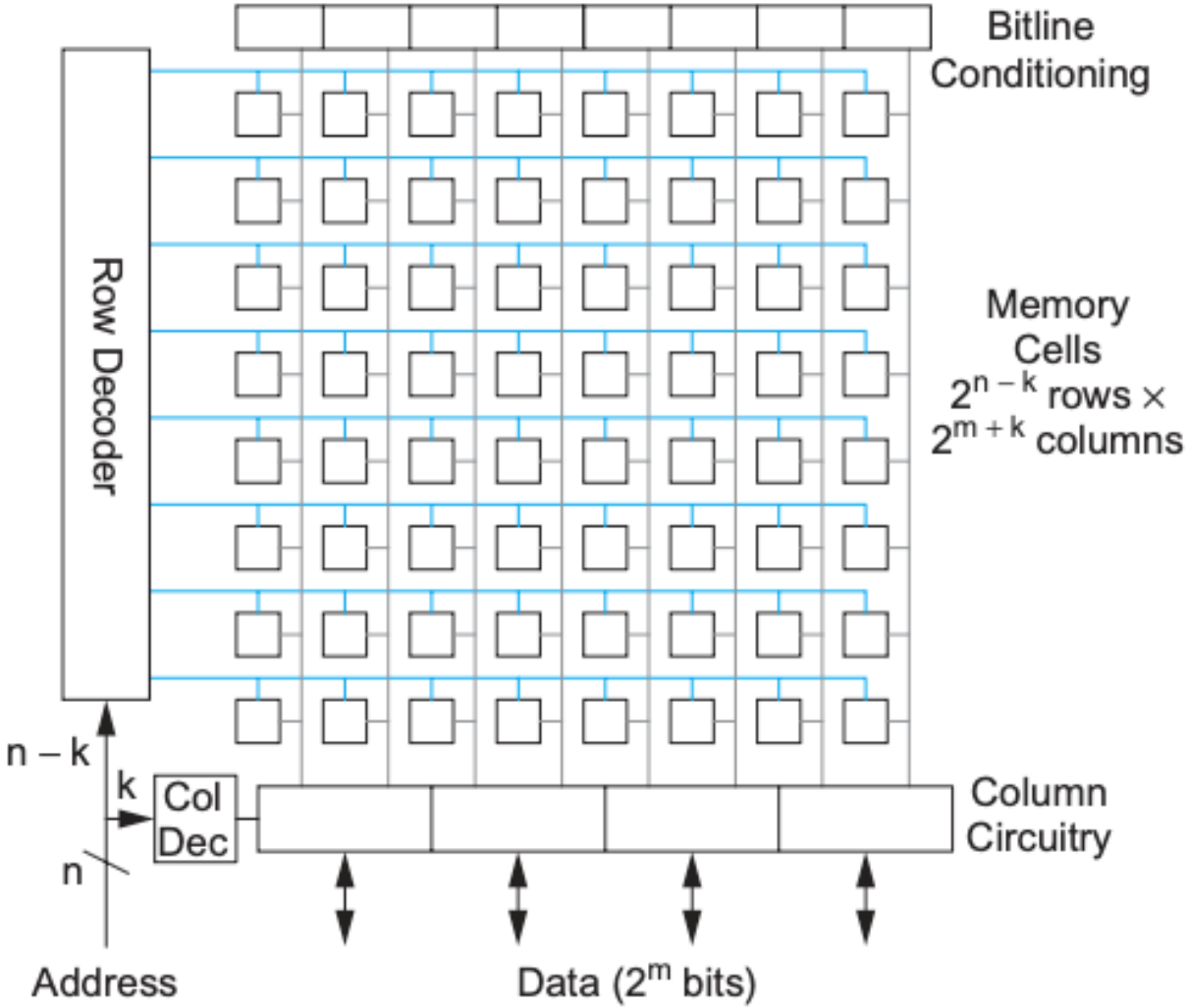

W&H p499-500


Read operation for SRAM cell

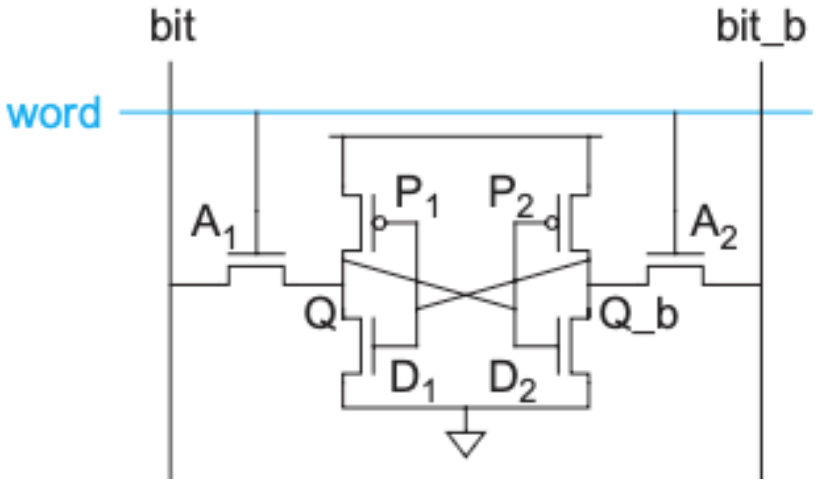


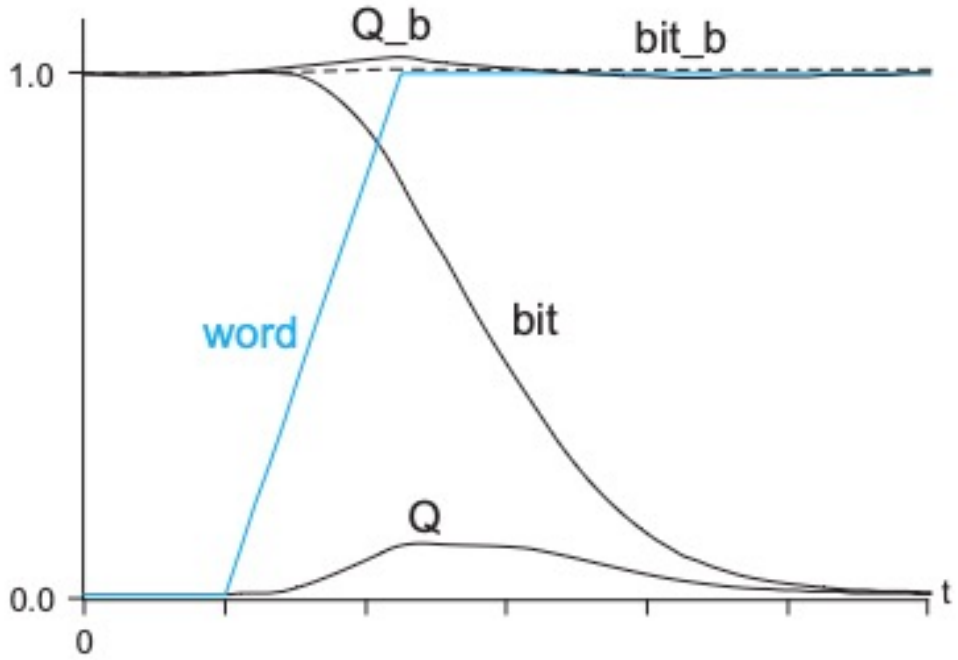

W&H p500


Column Read Operation

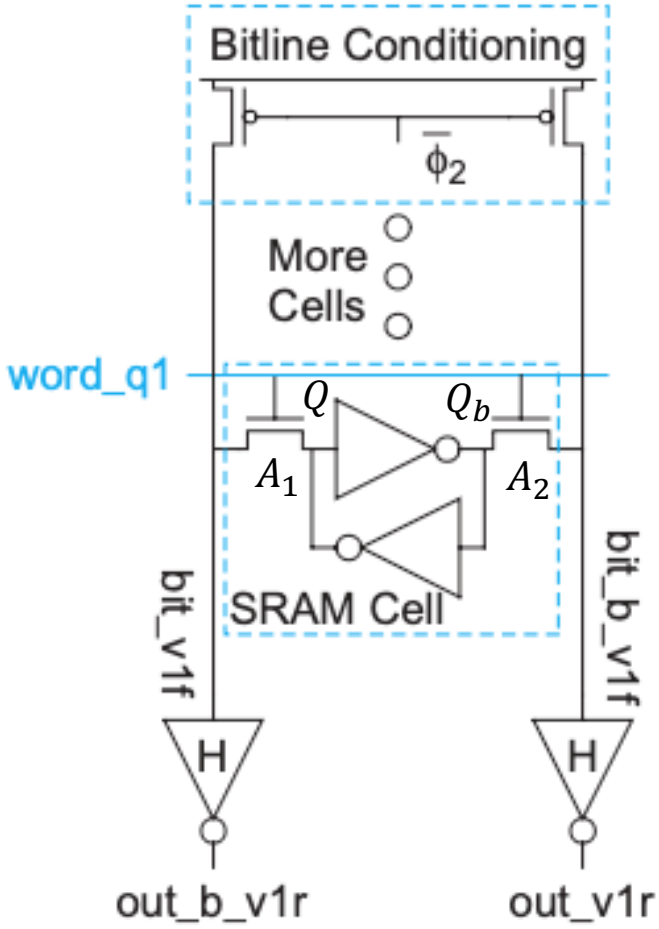


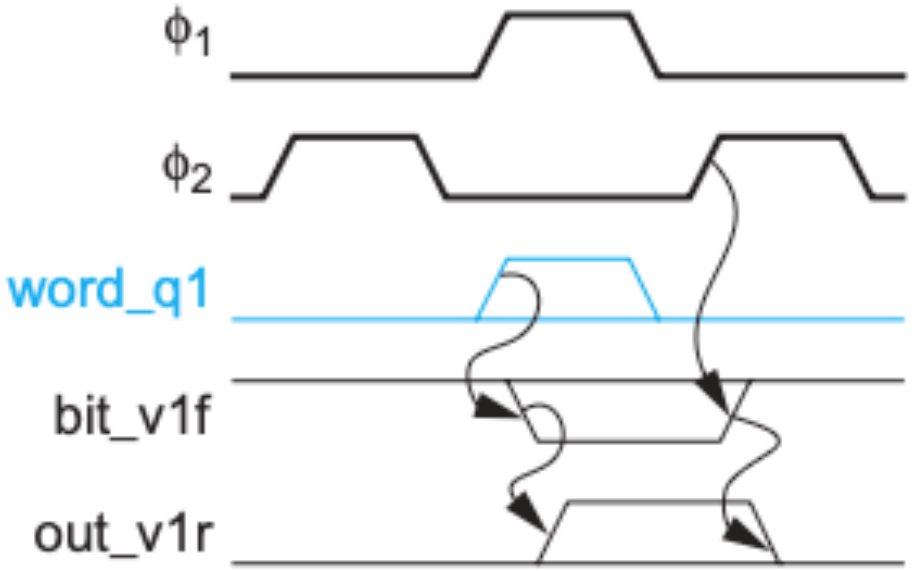


W&H p501

Write Operation

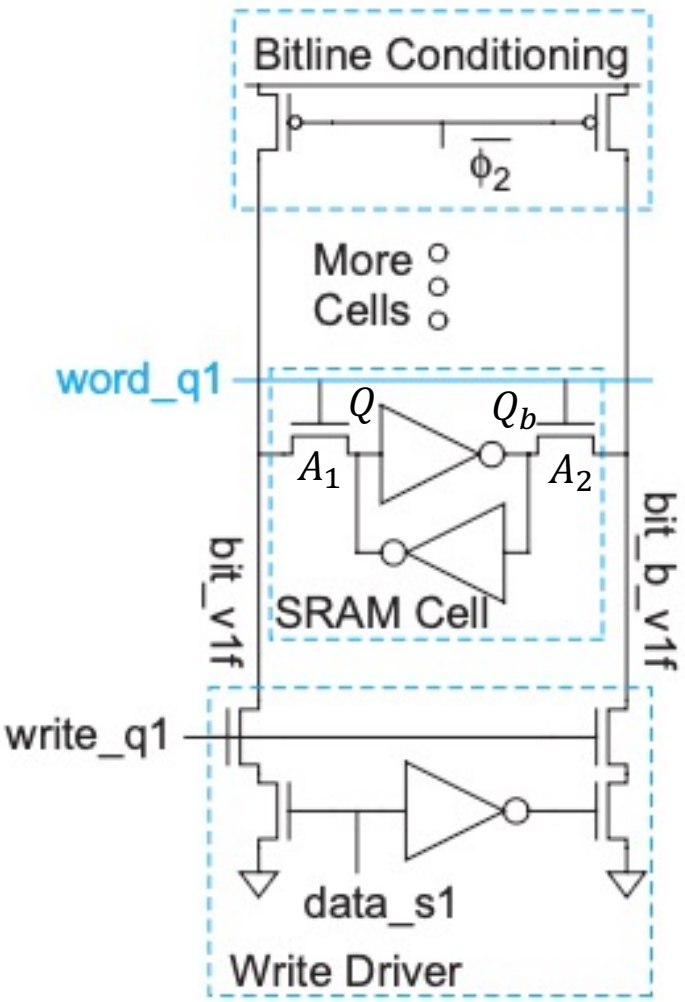


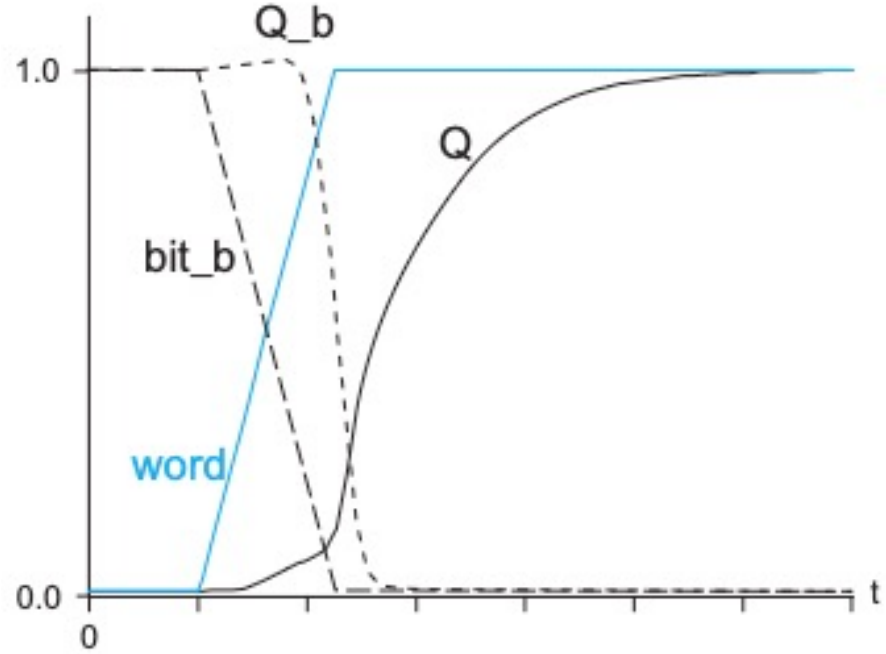


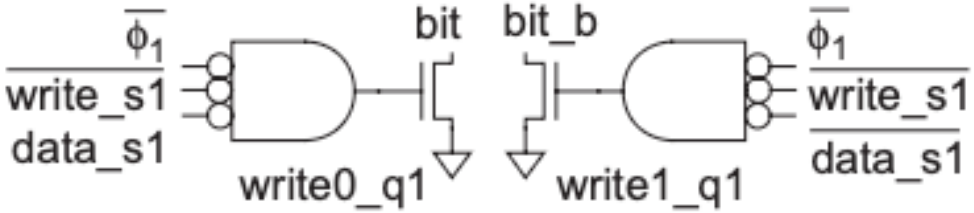

W&H p501


6T SRAM cell Layout (stick diagram)

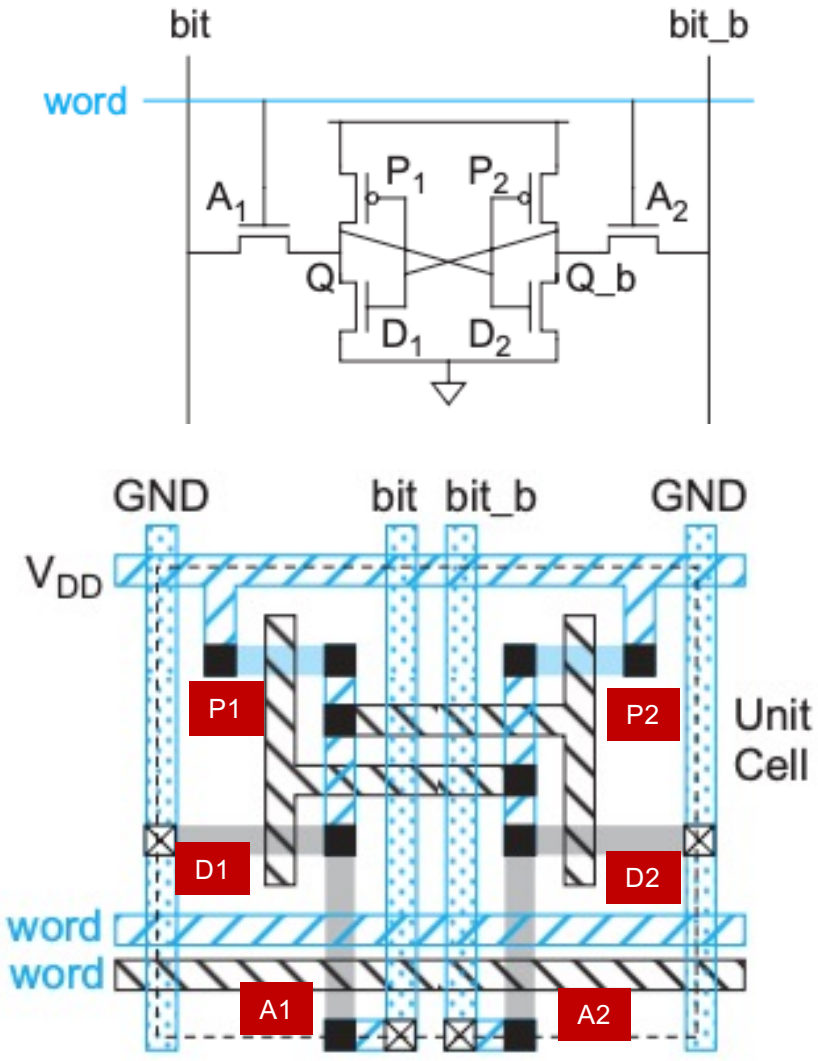

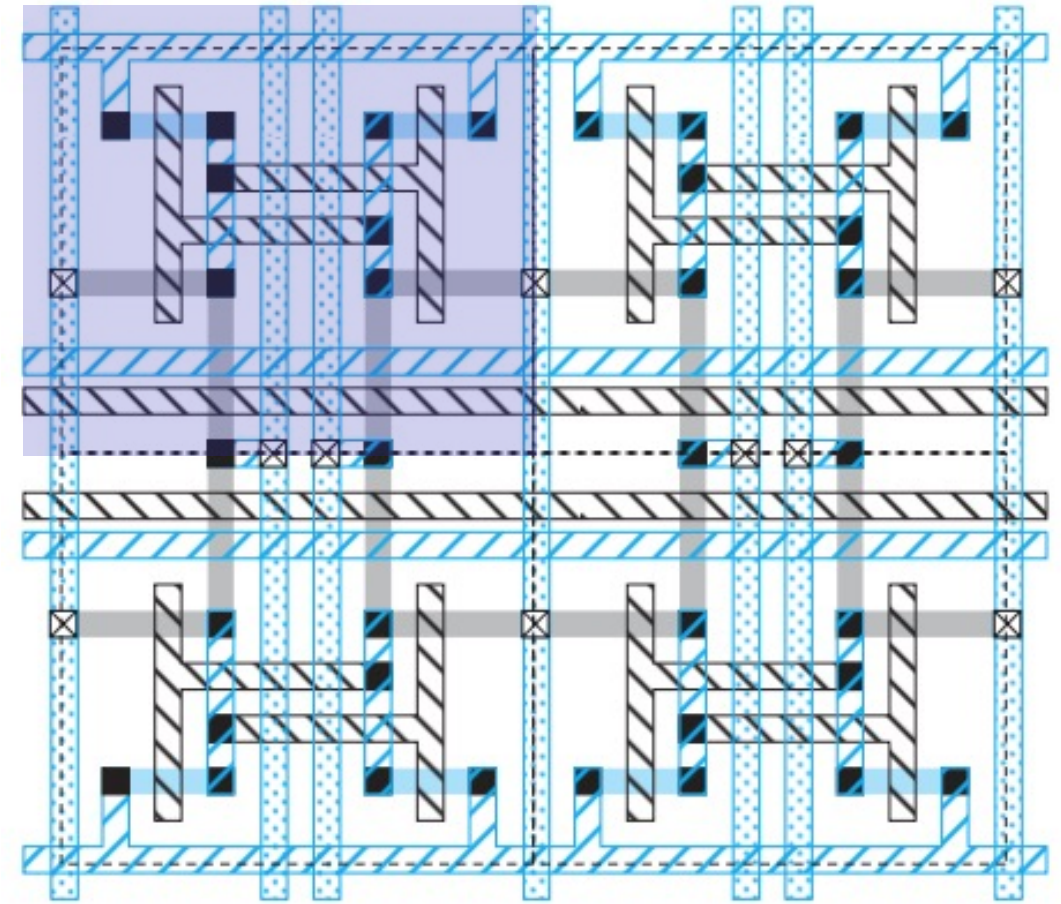


W&H p504


32 x 32 SRAM

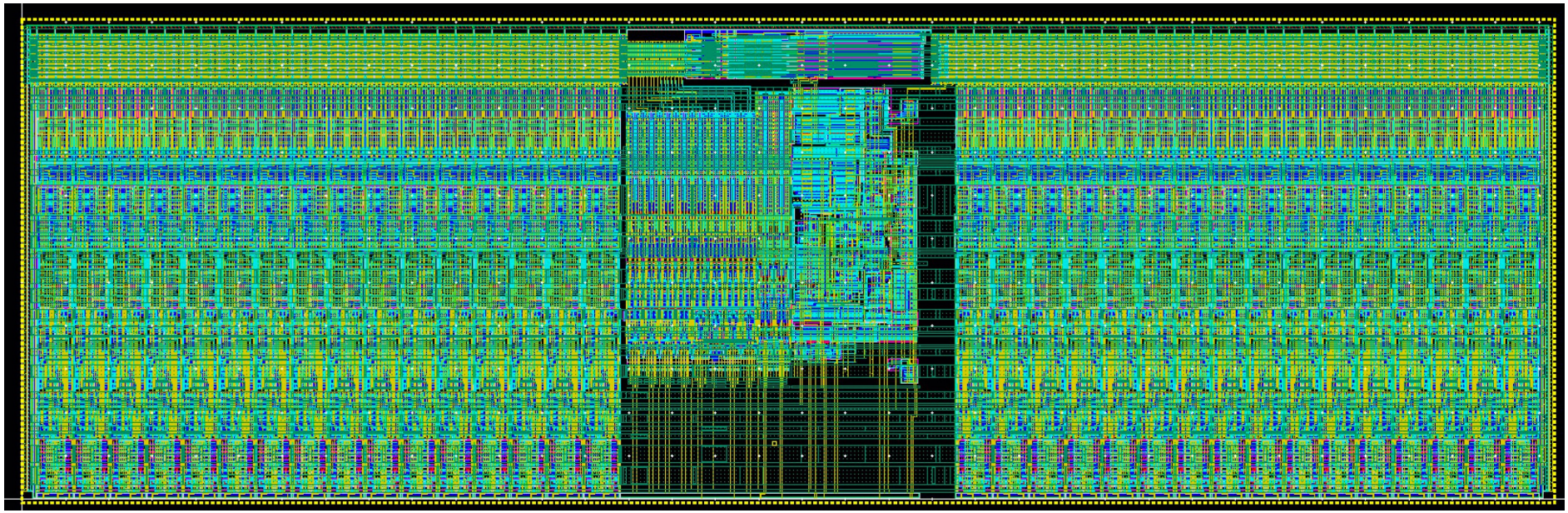


Zoom-in RAM cells

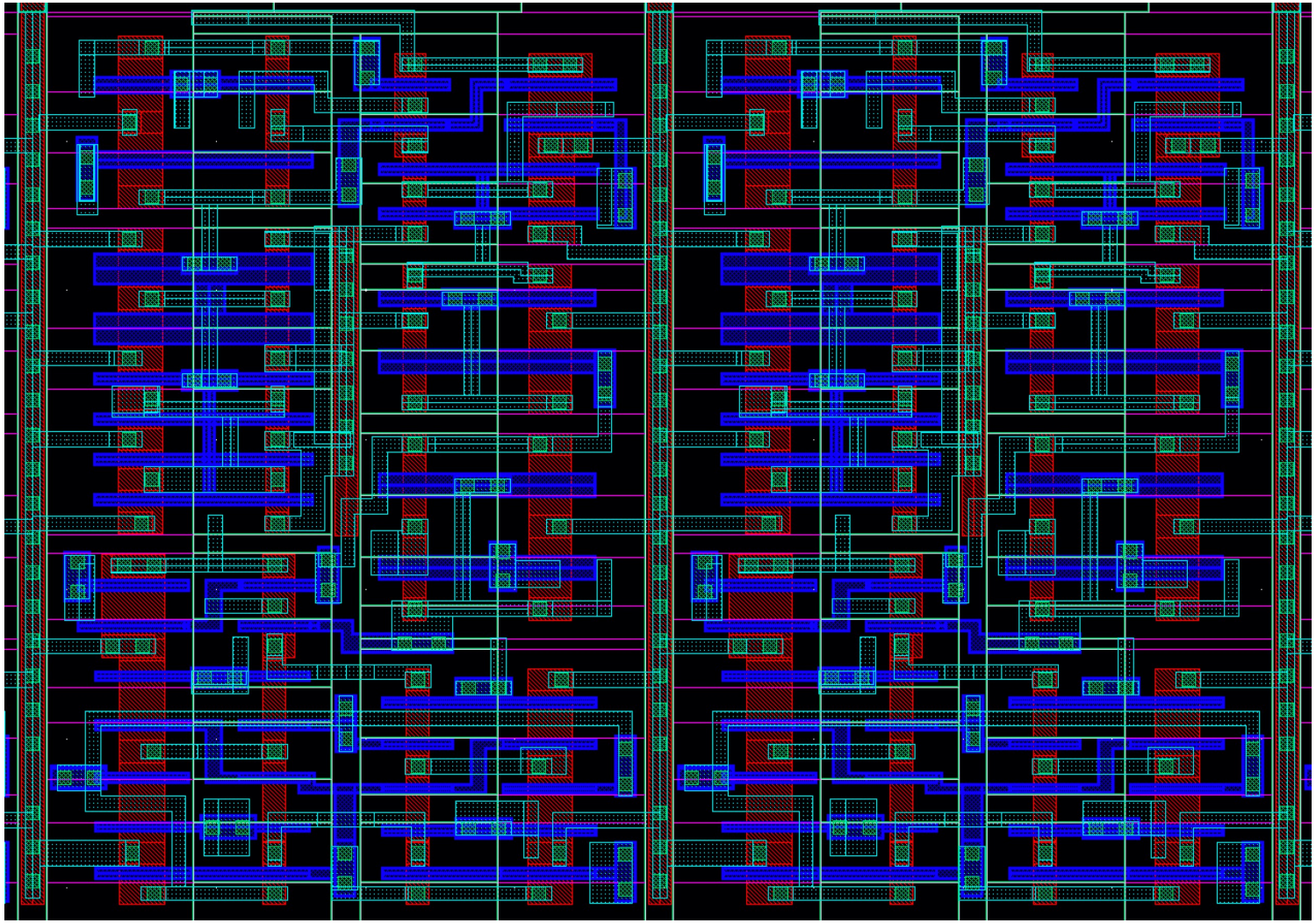


SRAM Scaling

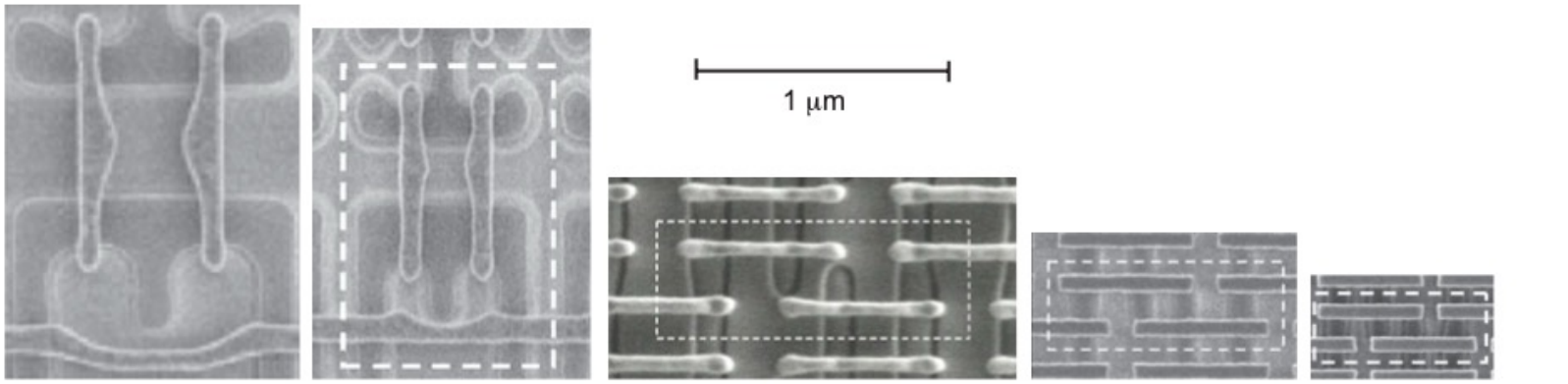


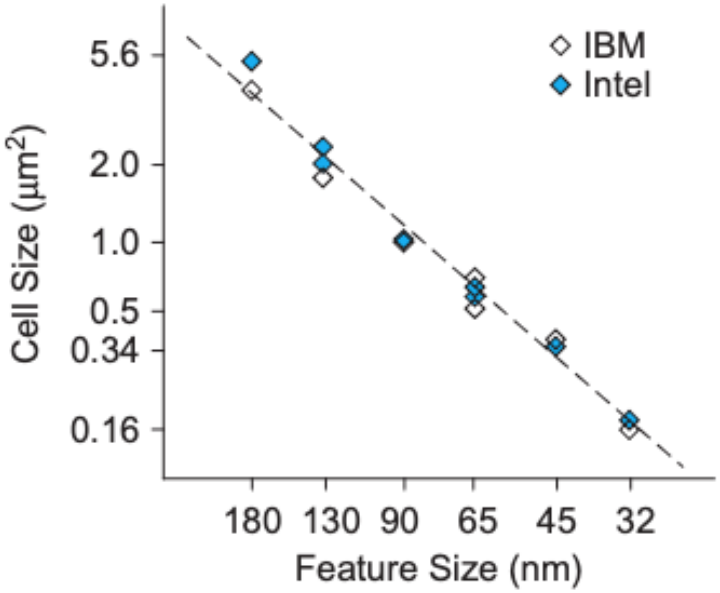


W&H p505

Row Decoder Circuits

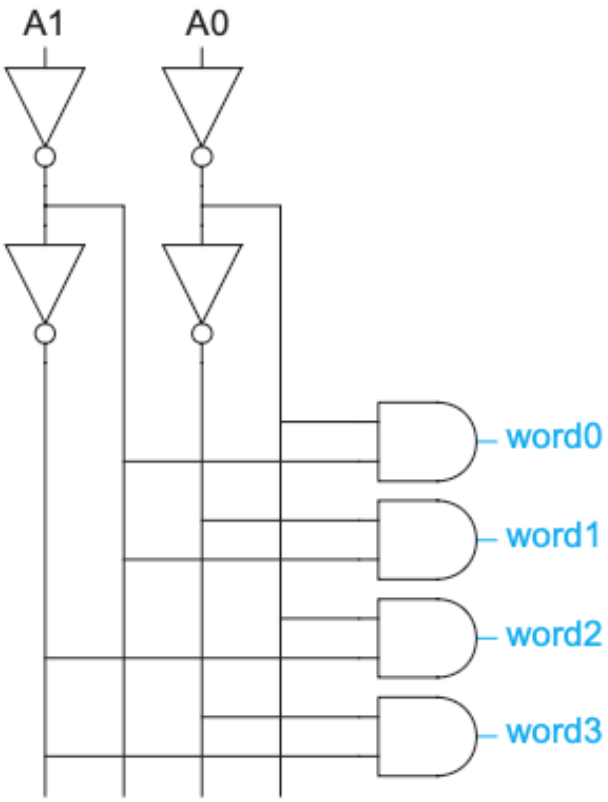

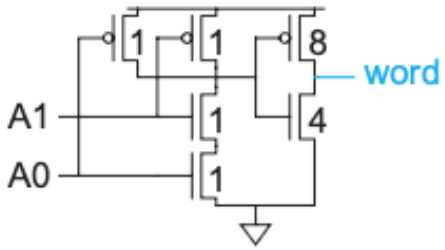


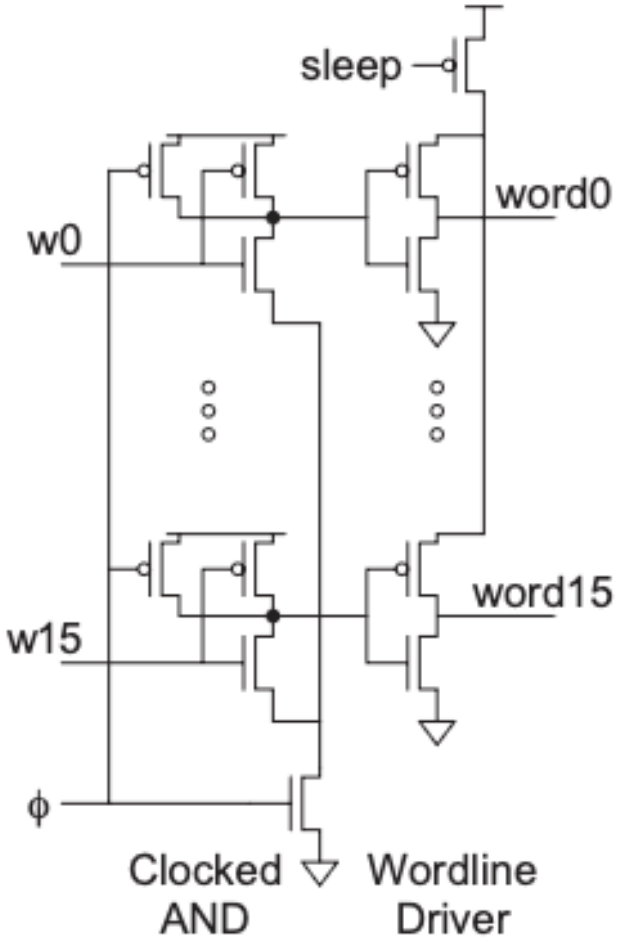

W&H p506-507


Sense Amplifier

Differntial Sense Amplifier

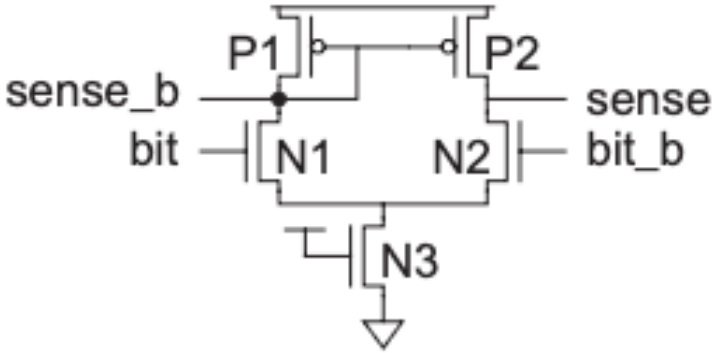

(a)


Clocked Sense Amplifier

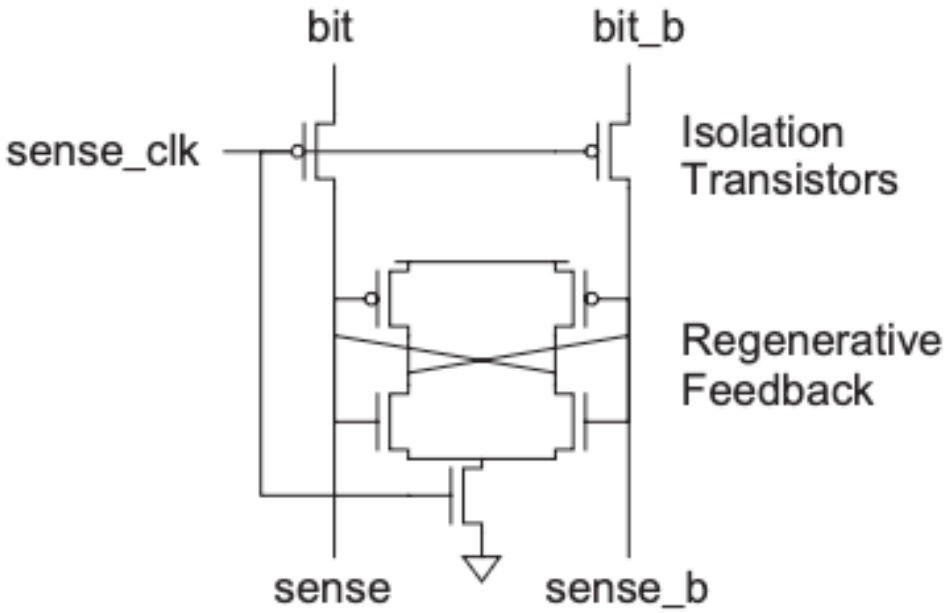

(b)


W&H p511

Differential Noise Reduction

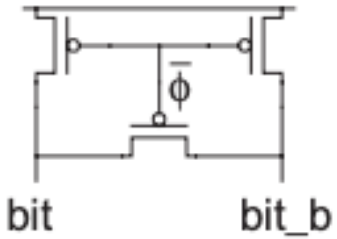

(a)

Bitlines equalization

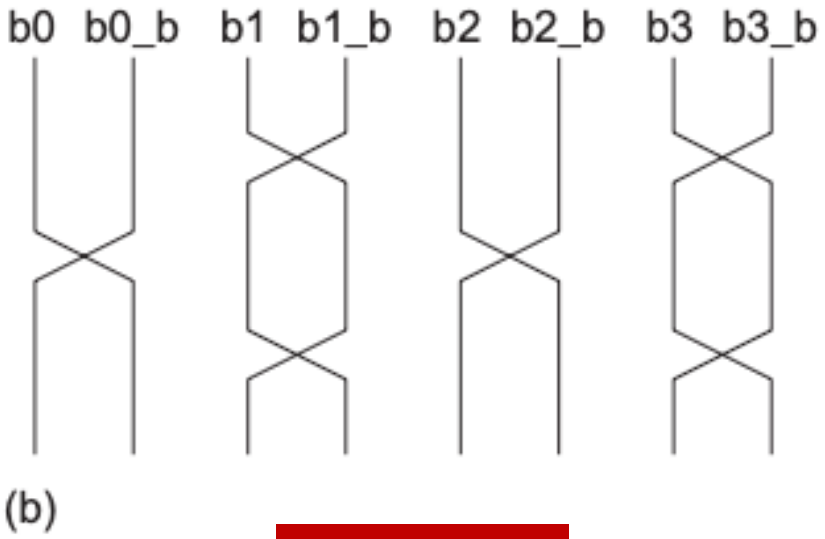



(b)


Bitlines twisting

W&H p513

Multiport SRAM

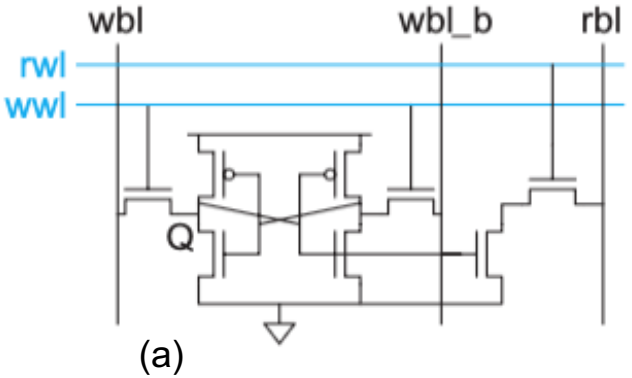

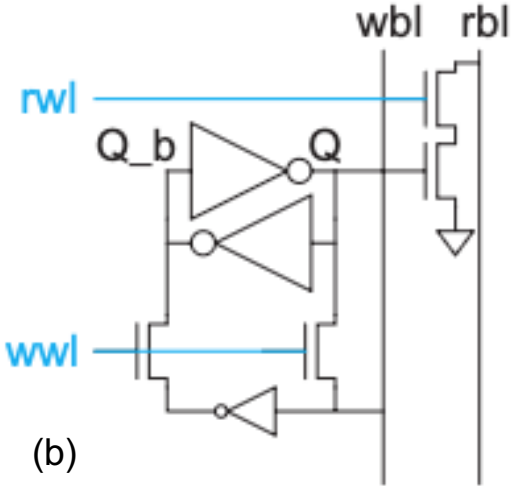


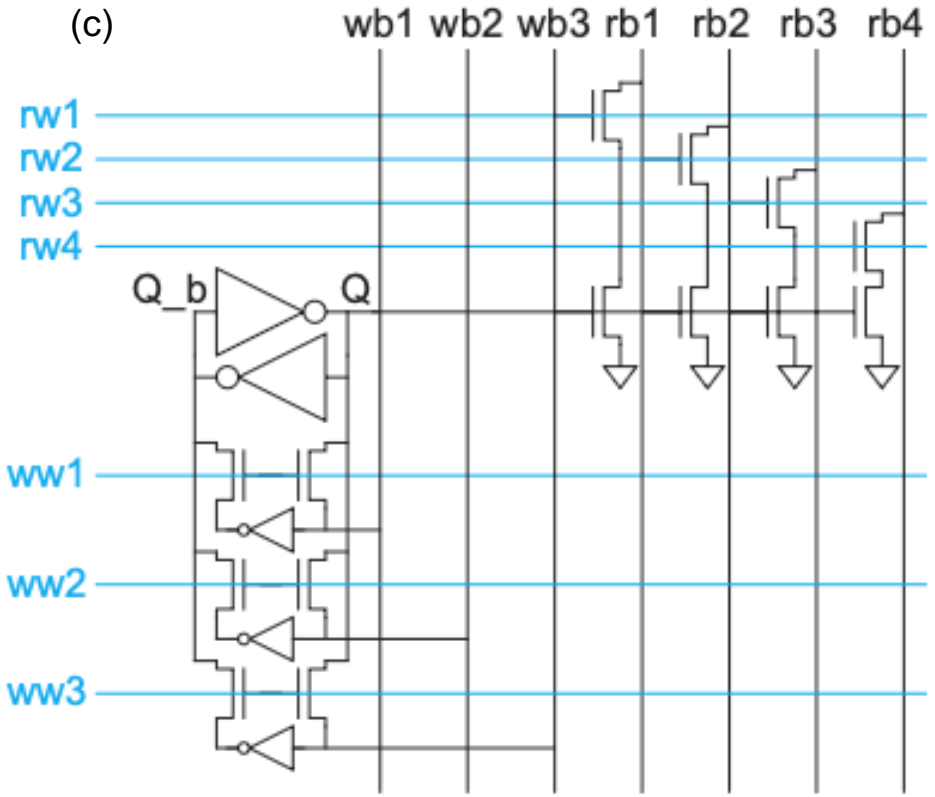



W&H p514-515


DRAM cell

Trench capacitor

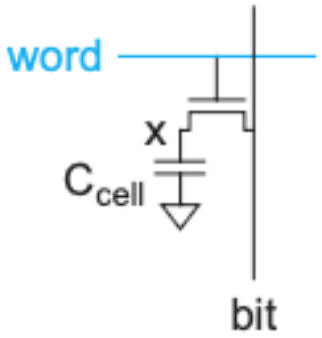

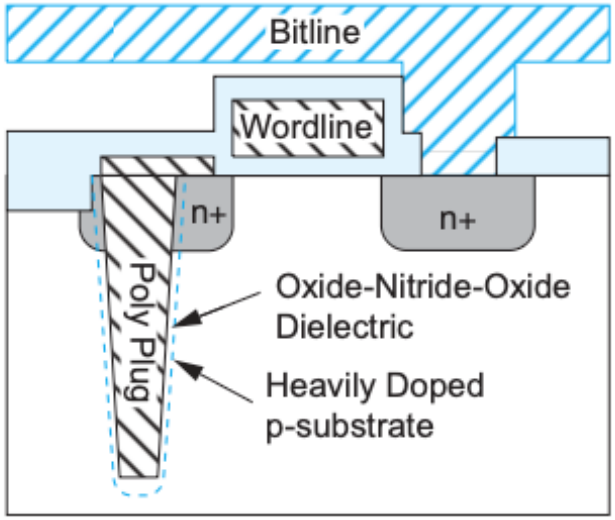

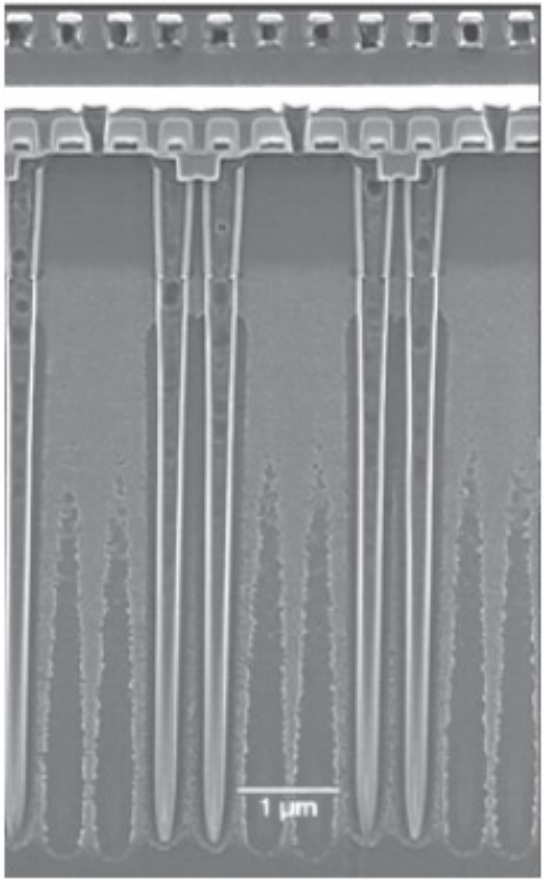

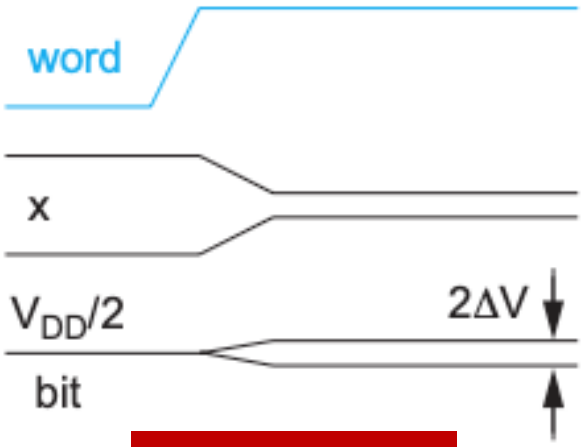

VDD/2 precharge


$$\Delta V = \frac{V_{DD}}{2}\frac{C_{cell}}{C_{cell}+C_{bit}}$$

Charge sharing


W&H p522-523

DRAM array

Open bitline

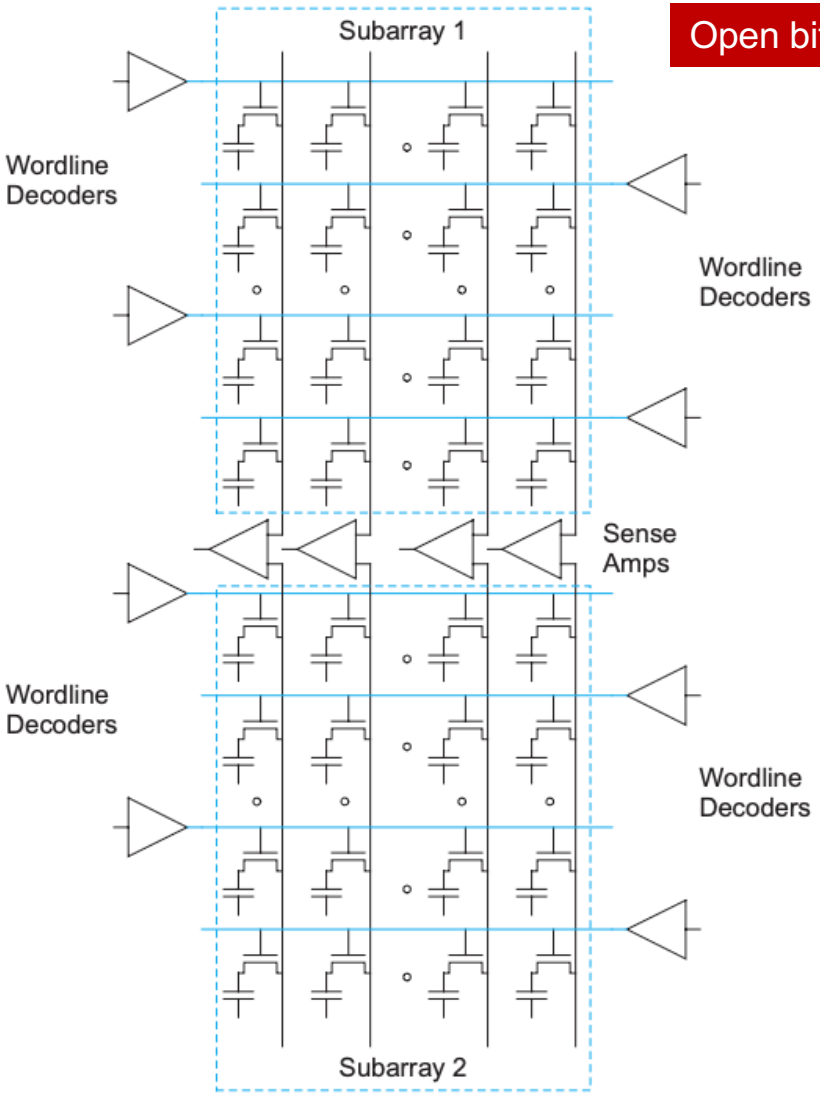


Folded bitline

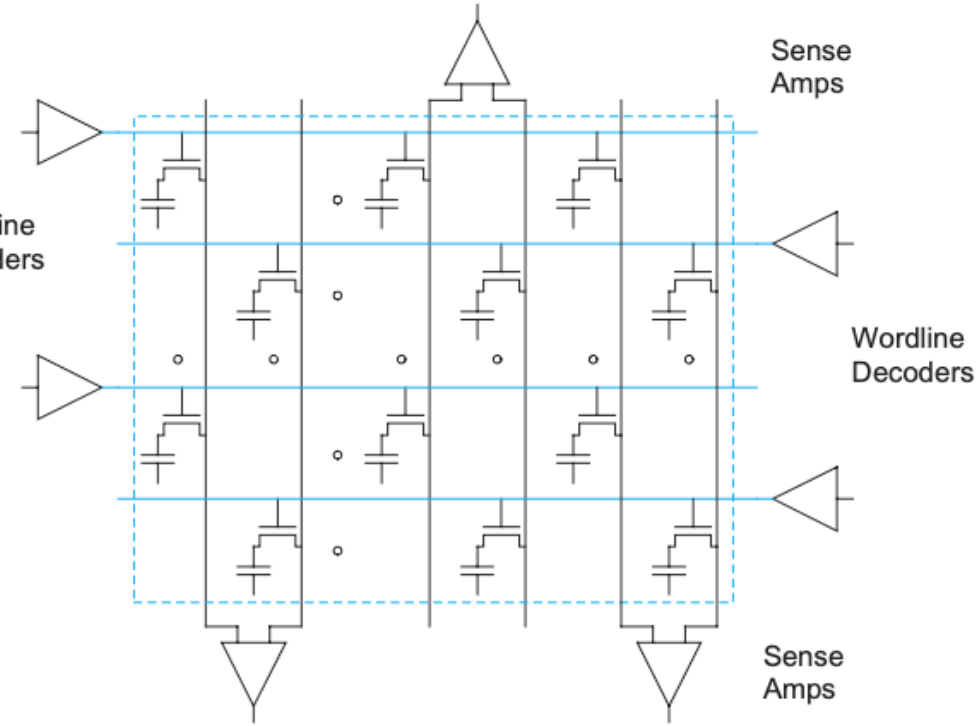

- Neighbouring bitline provide reference.
- Reduce noise sensitibity


W&H p524

Folded Bitline Layout

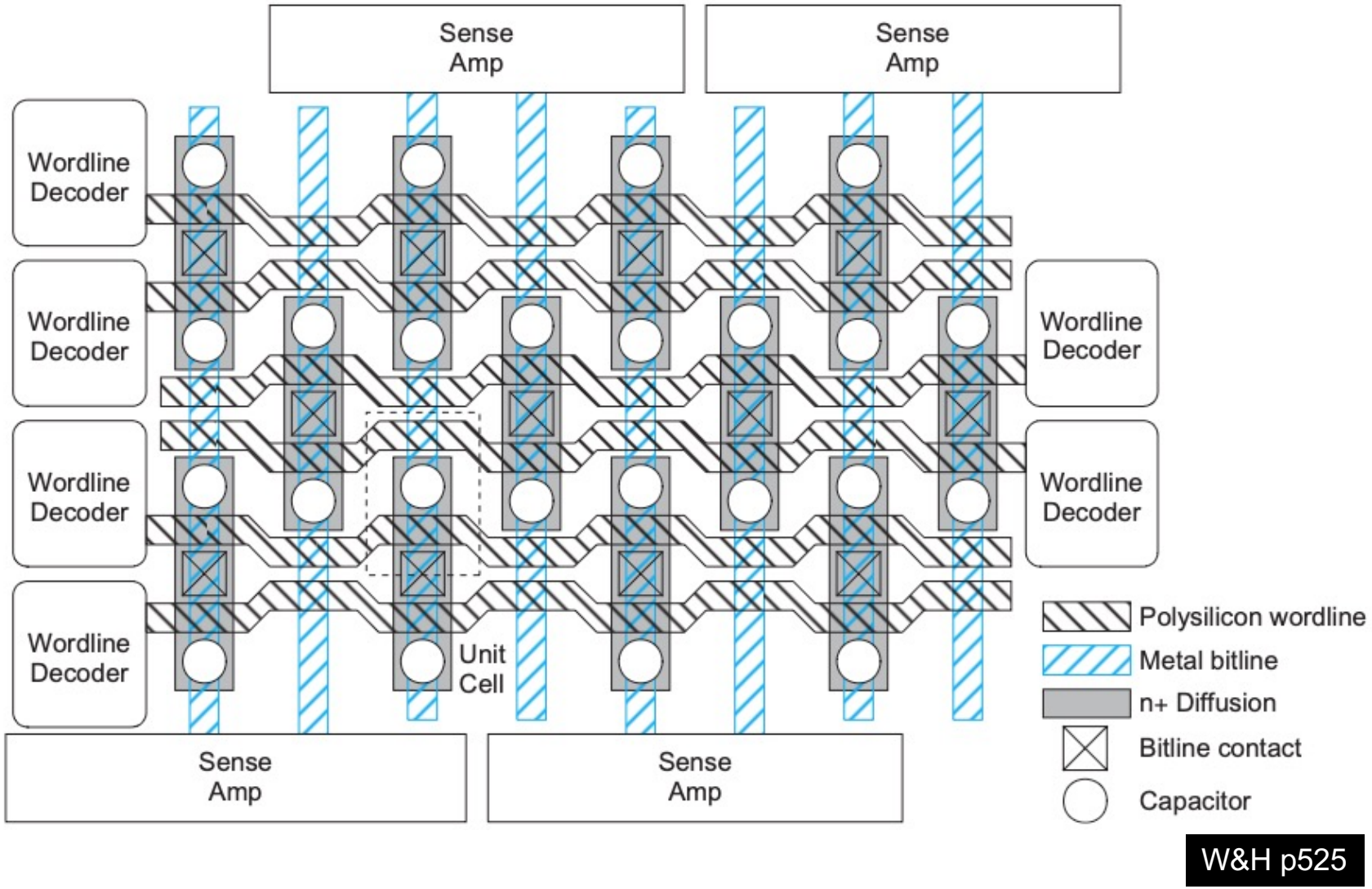


W&H p525

Pseudo nMOS ROM Circuit

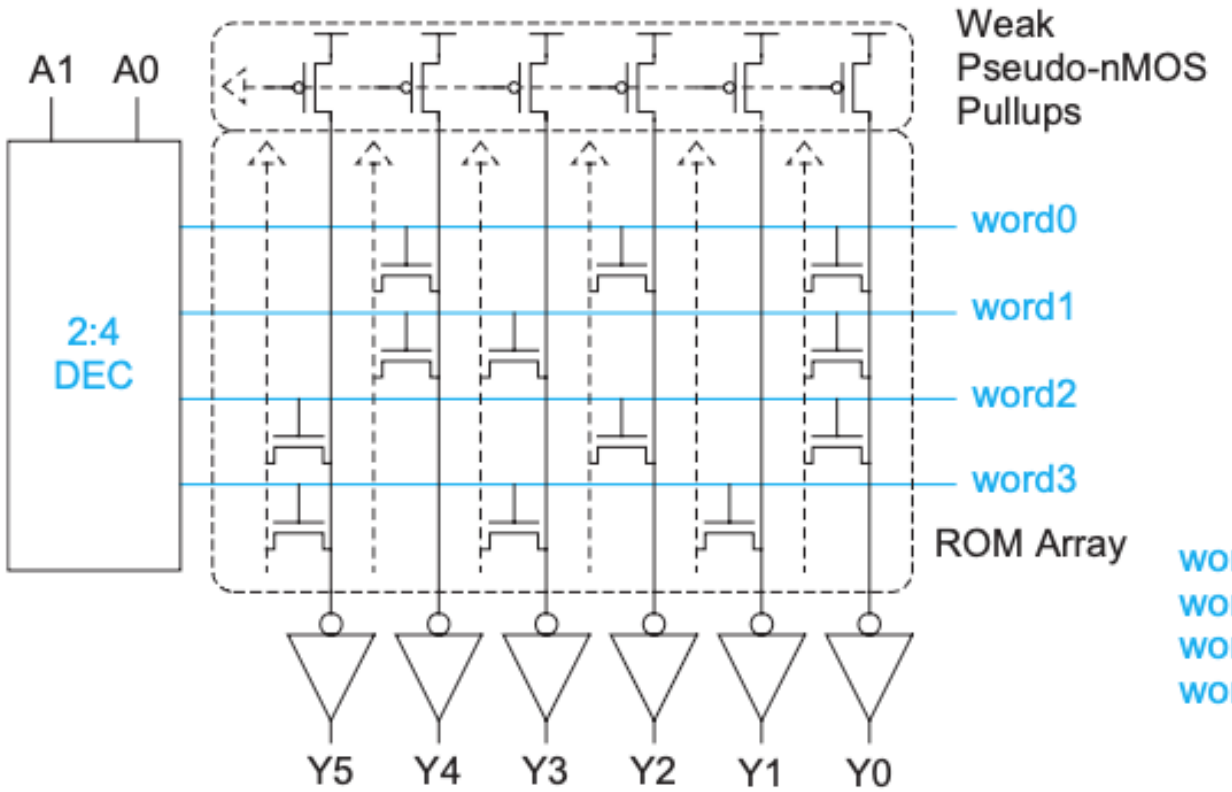


4-word by 6-bit ROM

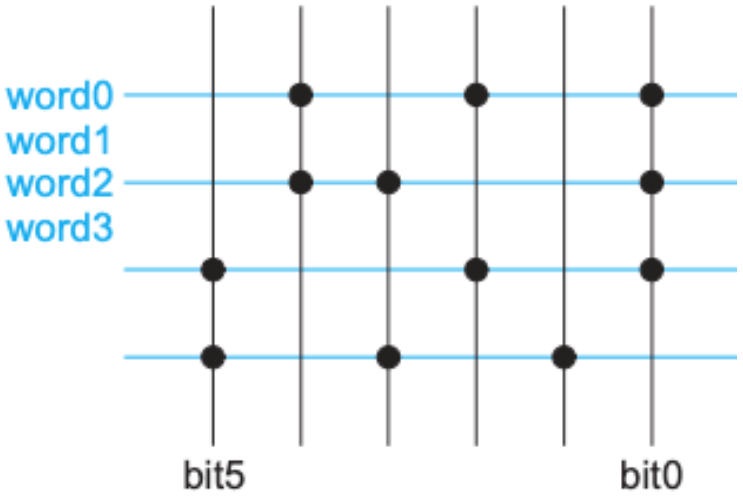
```
word0: 010101
word1: 011001
word2: 100101
word3: 101010
```



W&H p527


Flash Memory Cell

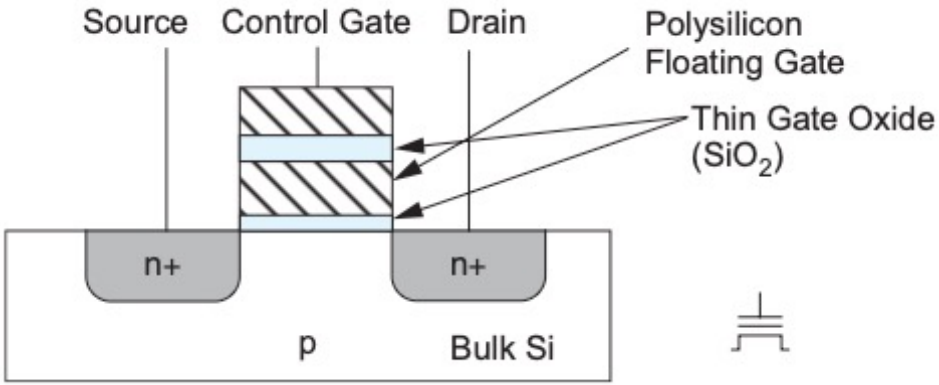

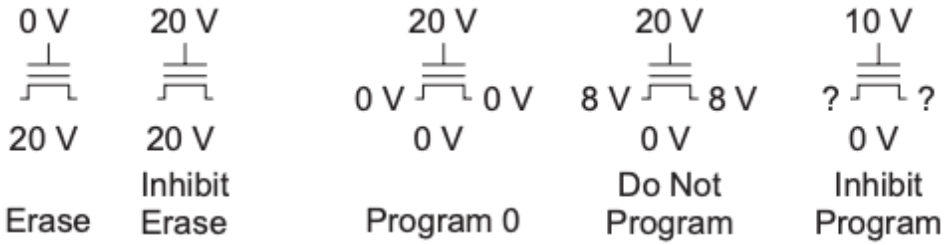


W&H p531

Flash Memory Array

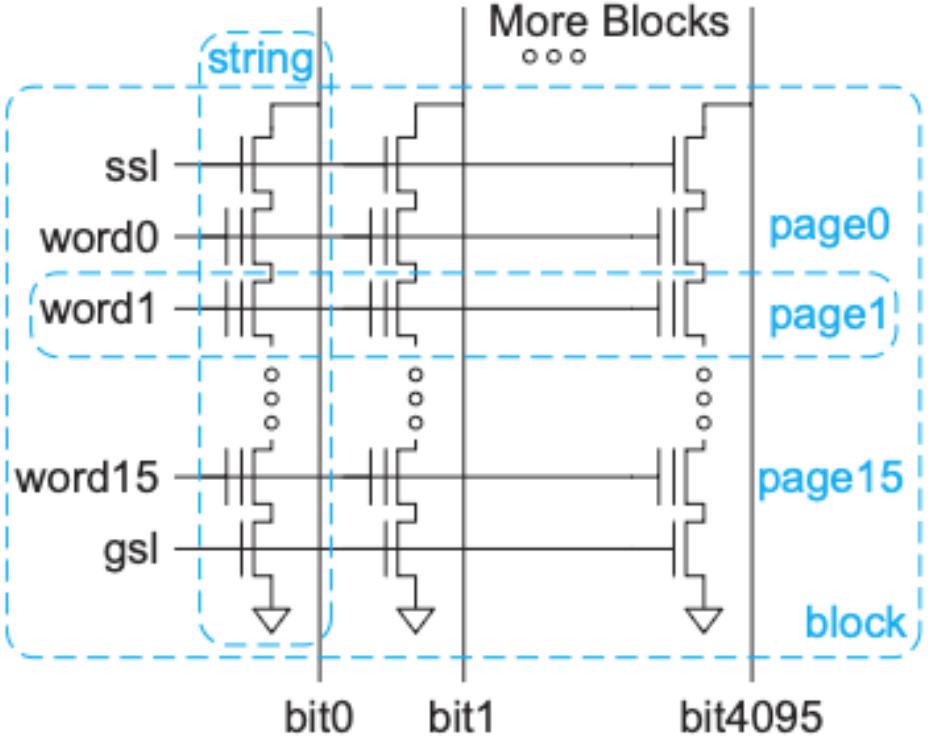


Each cell can store multibit value!

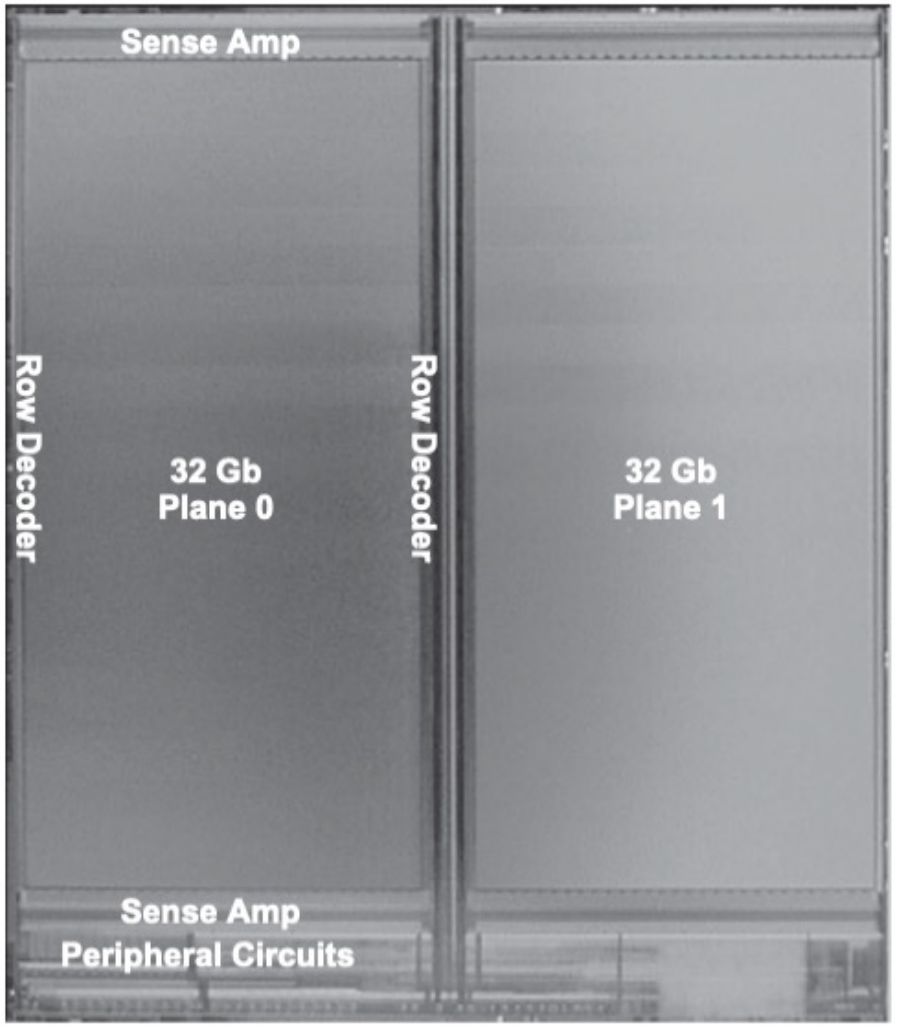


W&H p531

Shift Registers

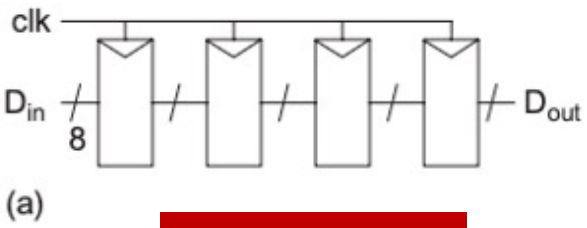


8-bit 4-stage SR

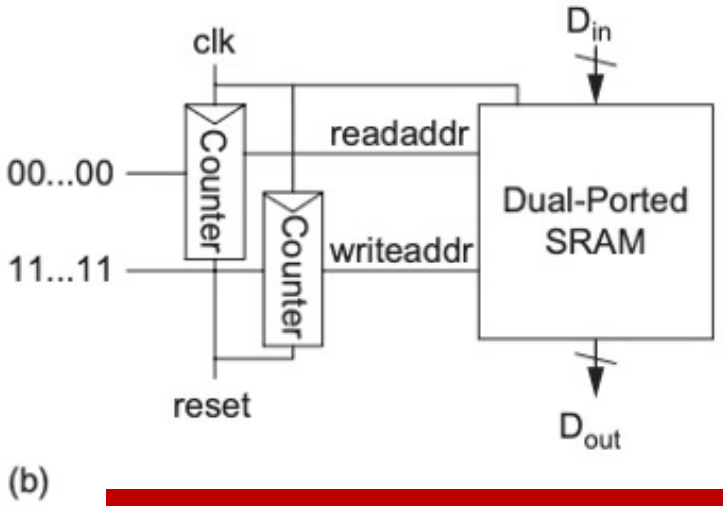


SR implemented with SRAM and counters

SR as tapped delay for DSP

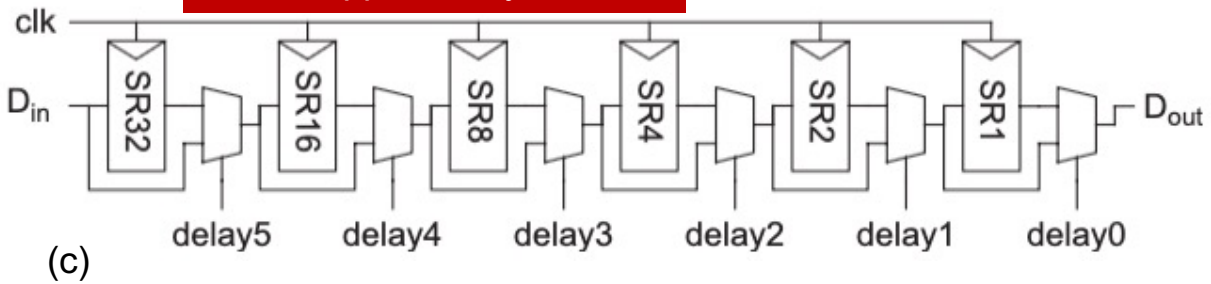


W&H p534

Delay Line and FIFO

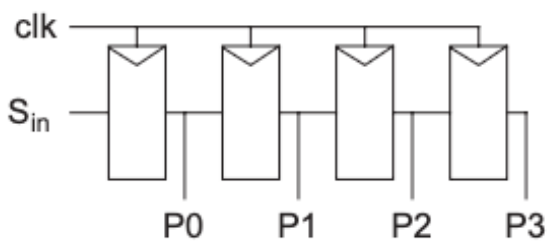


SIPO memory

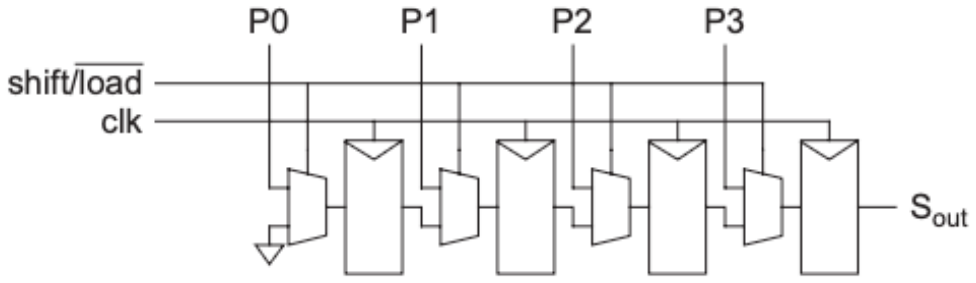


PISO memory


FIFO buffer

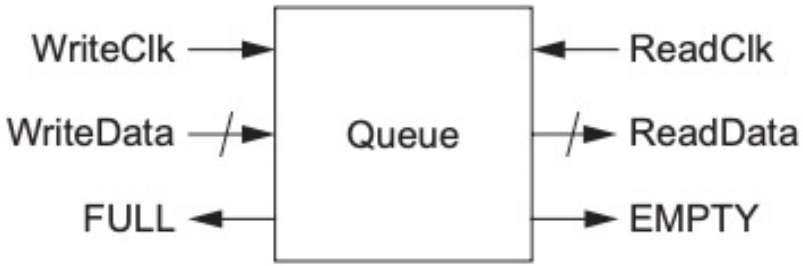

W&H p534


Content Addressable Memory (CAM)

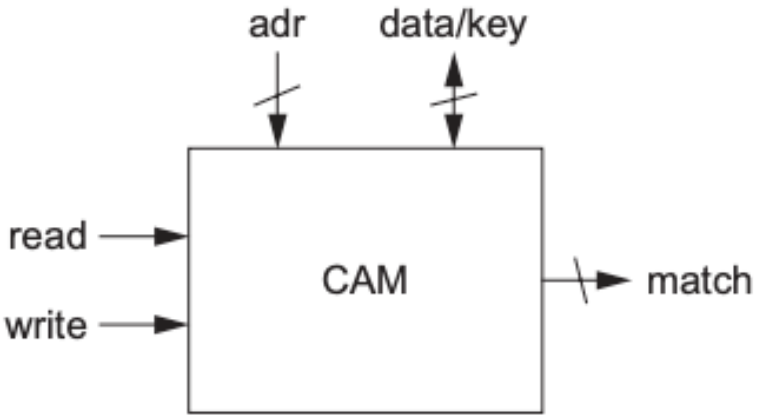


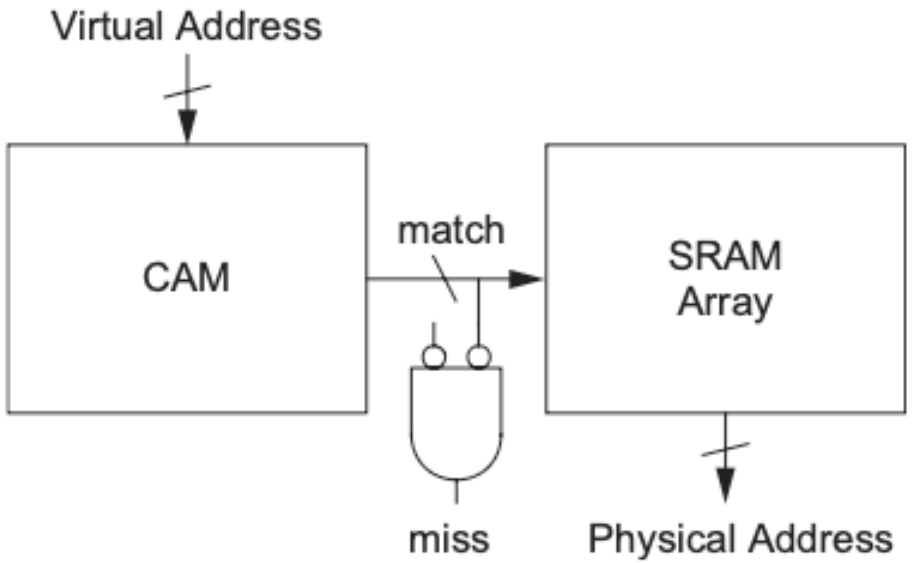

W&H p535


CAM Circuit (1)

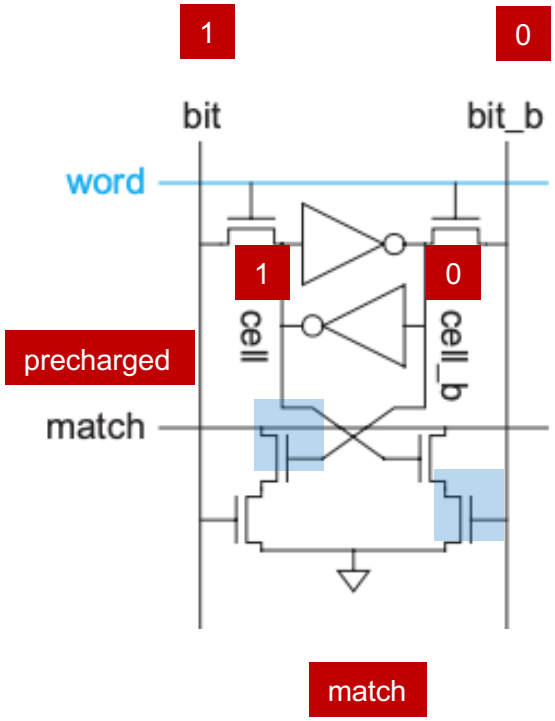

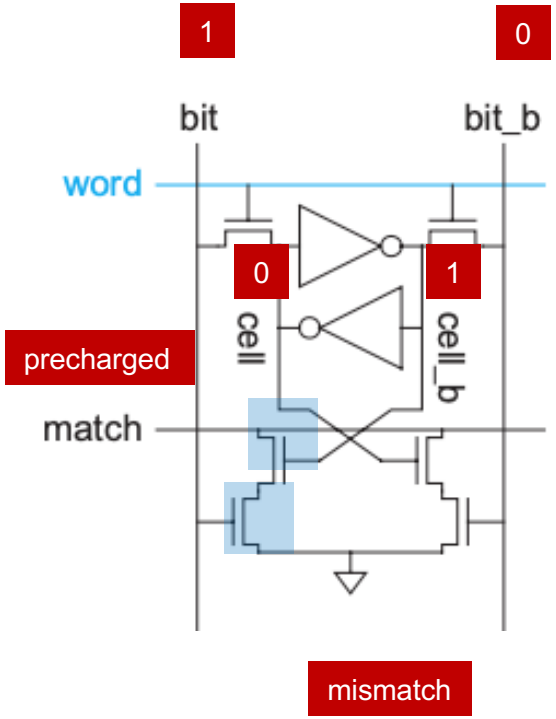

W&H p535

CAM Circuit (2)

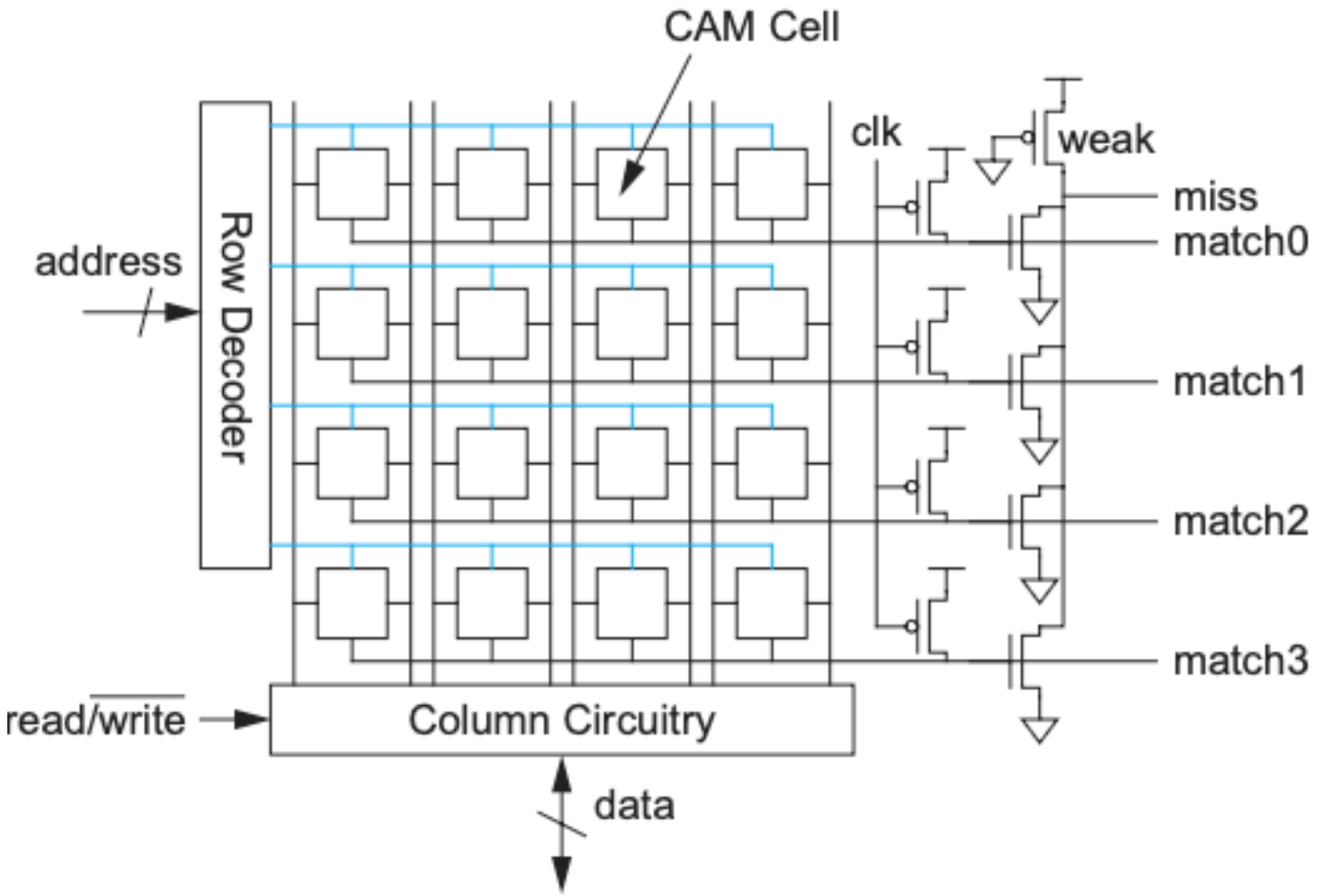

W&H p535